



VHDL

System ASIC Design Lab.

:

jcho@asiclab.inchon.ac.kr



Chap. 1

Chap. 2


Chap. 3 Digital System VHDL Modeling

Chap. 4 Test Bench Model






Chap. 1

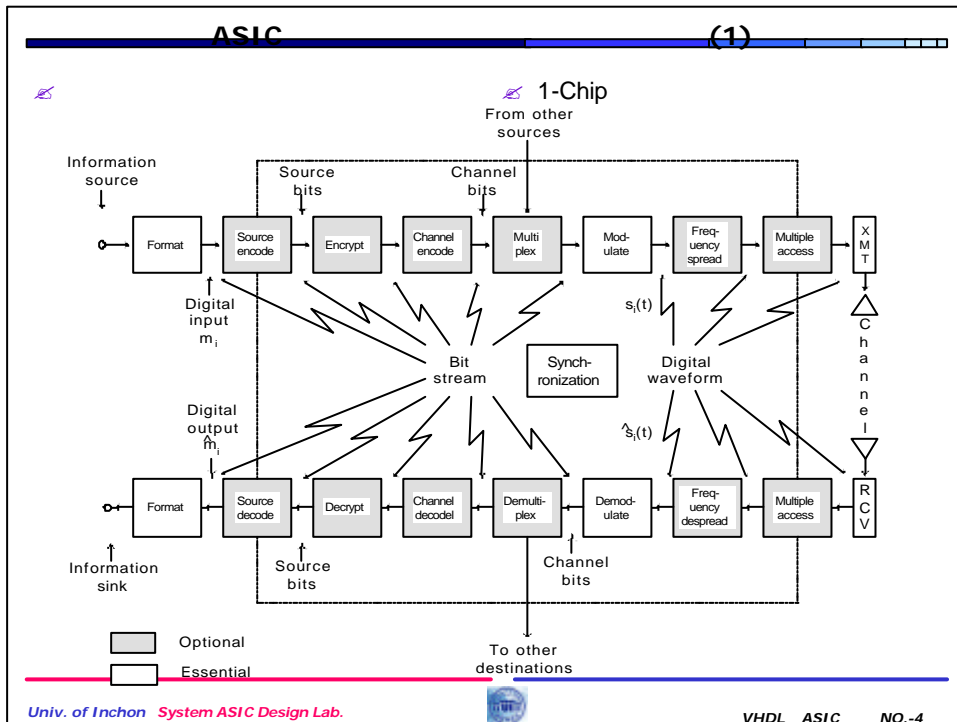

Wireless Audiovisual Terminal


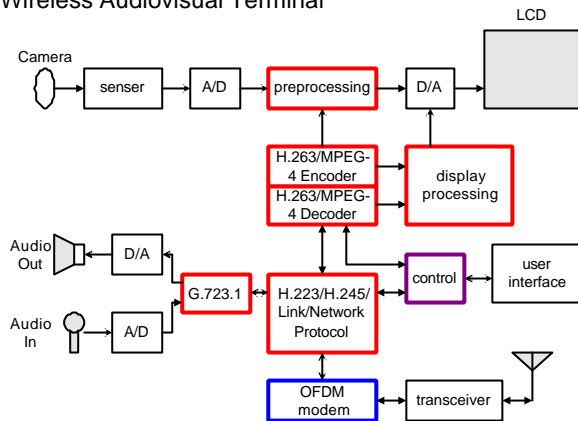


- ⌘ H.324 CODEC : Video Audio Data
- ⌘ Digital Communication Module : Data , Error
- ⌘ Micro-Controller : 16-Bit Processor Camera, LCD Interface Chips
- ⌘ Analog Front End Module : A/D, D/A

- ⌘ System Level
- ⌘ Behavioral Level
- ⌘ RTL Level
- ⌘ Logic Level
- ⌘ Circuit Level
- ⌘ Layout Level

Level	Graphical	Representation
System Partitioning, Pipelining		HDL, Graphical specifications
Behavioral Scheduling, Allocation		HDL, Bubble diagrams
RTL State Machines, Logic and RTL Multi-level, 2-level Optimization		Logic equations, HDL, Gates
Logic Technology mapping/translation		Layout CIF/GDSII
Implementation Place and Route		Layout CIF/GDSII

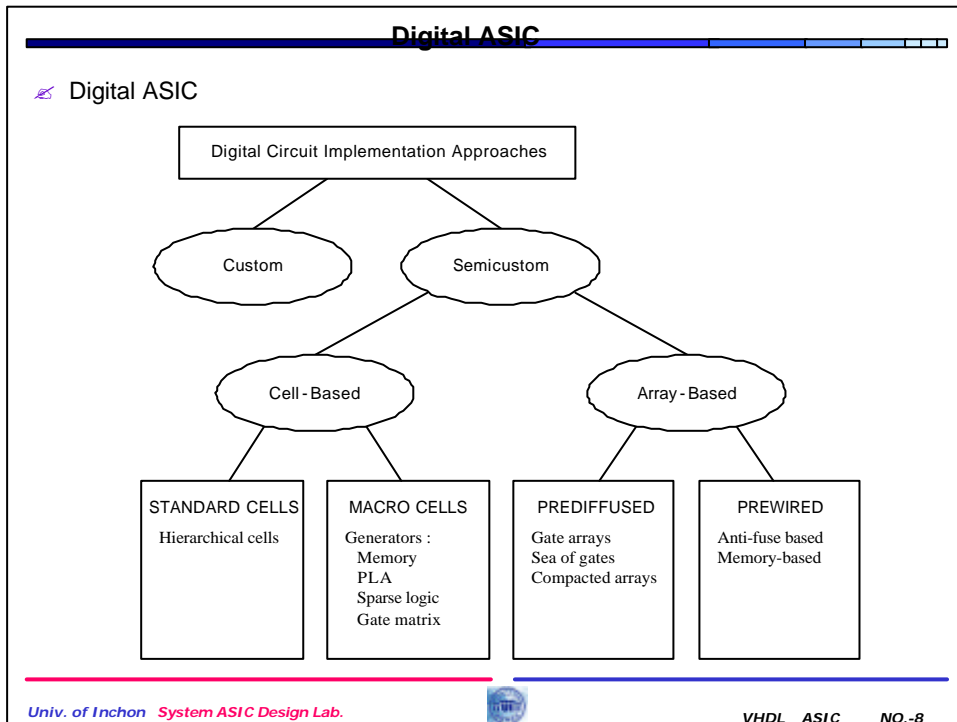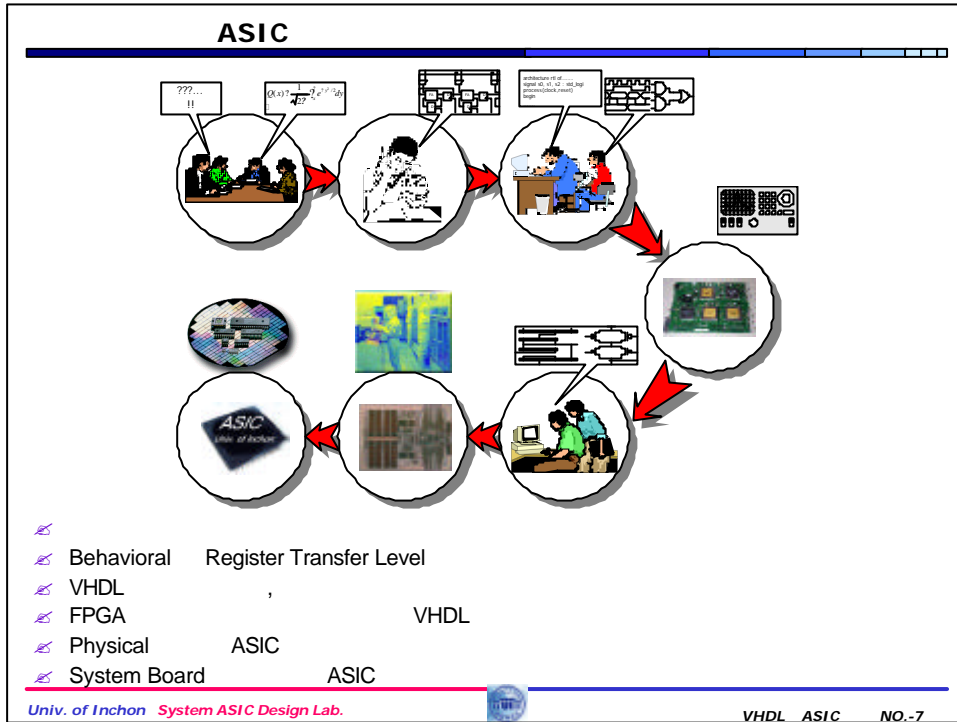- ⌘ Graphic Diagram
- ⌘ (HDL : Hardware Description Language)




Digital ASIC

ASIC

	<i>Custom</i>	<i>Cell-based</i>	<i>Prediffused</i>	<i>Prewired</i>
Density	Very High	High	High	Medium - Low
Performance	Very High	High	High	Medium - Low
Flexibility	Very High	High	Medium	Low
Design time	Very Long	Short	Short	Very Short
Manufacturing time	Medium	Medium	Short	Very Short
Cost - low volume	Very High	High	High	Low
Cost - high volume	Low	Low	Low	High


Standard-Cell Design

Boding Diagram

 


Sea-of-Gate Design

✍️ Boding Diagram : FLEX Decoder Chip

 

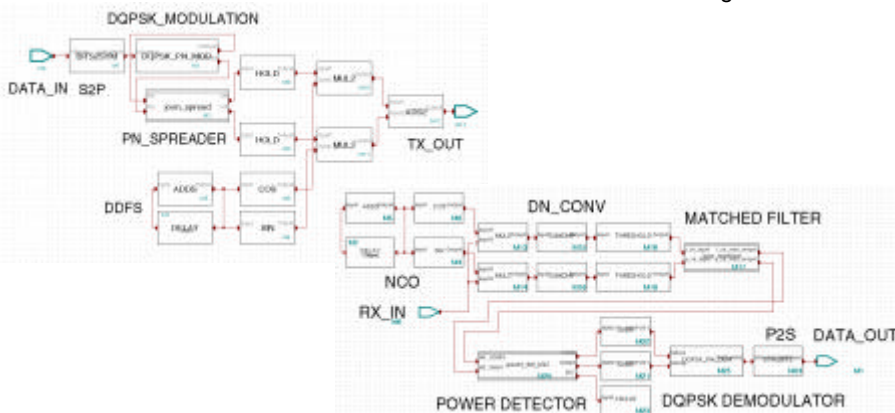
-1 : System(Algorithm) Level

- ✍️ C, MATLAB, SPW COSSAP System Level
- ✍️ library sub-block
- ✍️ system (, BER)
- ✍️ hardware complexity performance data-bus bit size
- ✍️ System Chip
- ✍️ COSSAP DS/SS Base Band MODEM Modeling



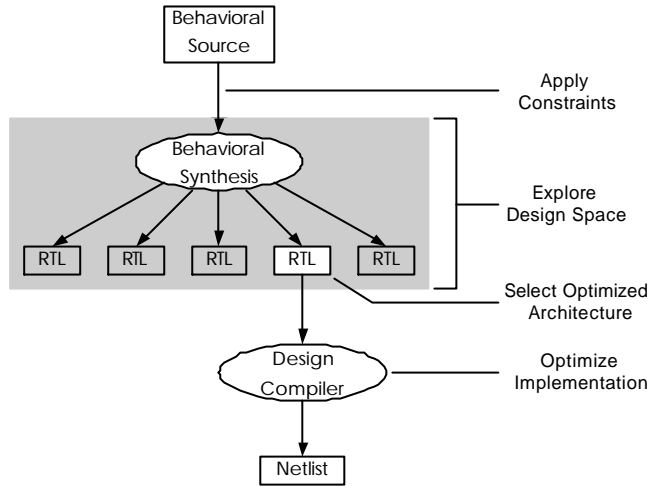
-2 : Behavioral Compiler

- System Level
- Behavioral Compiler
- 가 RTL
- Option
- RTL
- RTL



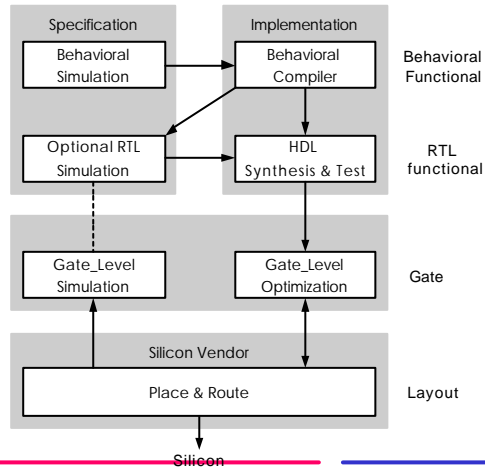
-2 : Behavioral Compiler Design Flow

- Behavioral Compiler
- Design Flow
- Operator to State Binding
- Variable to Register Binding
- Function Unit Sharing
- Control Logic
- FSM



-2 : Behavioral Compiler RTL


가 $\sqrt{a^2 + b^2} + \max((0.875x + 0.5y), x)$
 $x = \max(|a|, |b|)$
 $y = \min(|a|, |b|)$

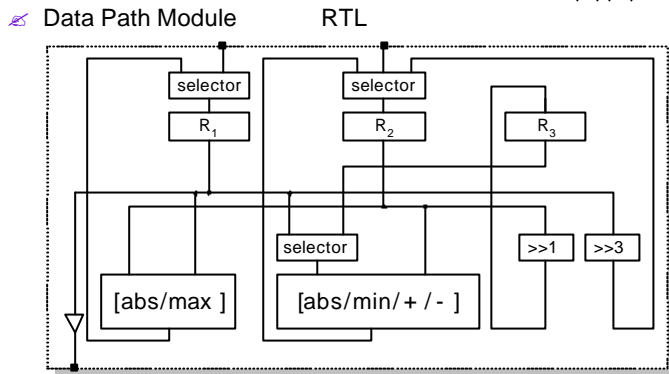

Controller Module RTL
 FSM Table Model


-3 : Register Transfer Level

RTL Target Architecture

 

- 3 : Register-Transfer Level

☞ Synthesis 가 VHDL Hardware

 

☞ Target Architecture


- ☞ : Basic Gates, Modular Units (mux, decoder, arithmetic units)
- ☞ : F/Fs, Registers, Counters, FSM(Finite State Machine)
- ☞ : ROM, RAM
- ☞ Bus : 3-Buffer

3 : Design Compiler

☞ Design Flow 3

- ☞ RTL
 - ☞ VHDL
 - ☞ Simulation
 - ☞ Gate Level
 - ☞ , , Power
 - ☞ Design Library : FPGA, ASIC
 - ☞ Component Delay
 - ☞ Timing Simulation
- ☞ Physical Design EDIF
 - ☞ FPGA Physical Design
 - ☞ FPGA Tool Compile
 - ☞ Device Option
 - ☞ Layout Data Simulation
 - ☞ Target Board Emulation
- ☞ ASIC
 - ☞ ASIC Physical Design
 - ☞ Design House EDIF
 - ☞ Wire Delay Simulation
 - ☞ Sign-off ASIC
 - ☞ Test Board 가

☞ Design Flow

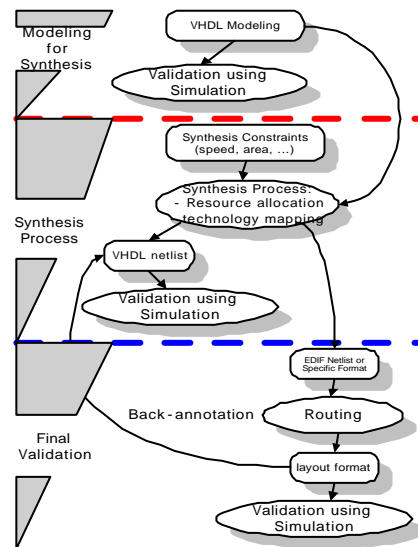



Design Entity
 Subprogram, , Component
 VHDL
 Interface
 Package Declaration Design Unit
 Sub-Program Algorithm
 Package Body Design Unit
 Package declaration + associated package
 package declaration
 package body
 Subprogram headers (declarations)
 algorithms of the subprograms

Univ. of Incheon System ASIC Design Lab. VHDL ASIC NO.-21

VHDL 57 Design Unit

Hardware 37 Unit
 entity declaration unit
 interface
 architecture body unit
 configuration declaration unit
 entity unit architecture unit
 simulation
 Software 27 Unit
 package declaration unit
 design entity
 package body unit
 subprogram
 27 Unit
 entity unit
 9-Value Package Visibility
 I/O
 architecture unit
 : Behavioral View Model
 : Structural View Model

 
 
Univ. of Incheon System ASIC Design Lab. VHDL ASIC NO.-22



VHDL Model (2)

Design Tree 1-Level VHDL

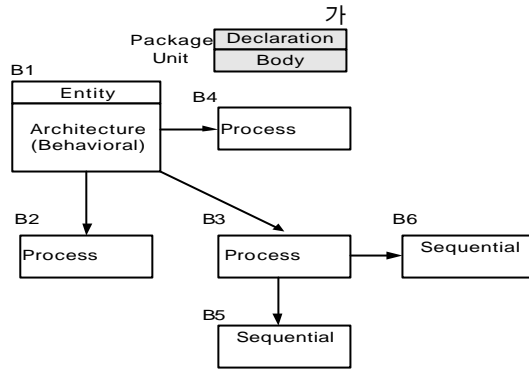 
- Root Design Node Entity Unit + Architecture Unit
- Root Design Node Concurrent VHDL



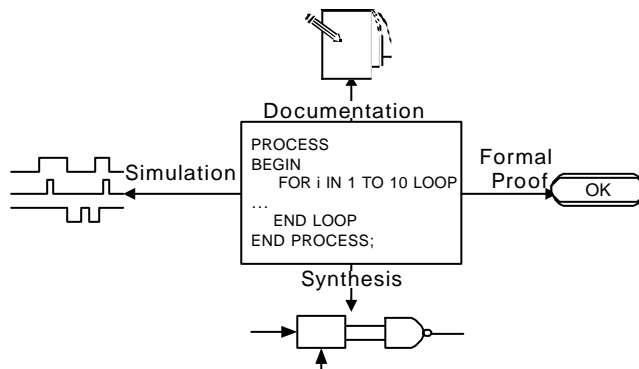
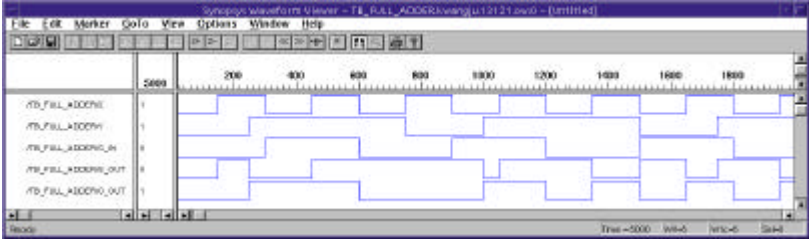
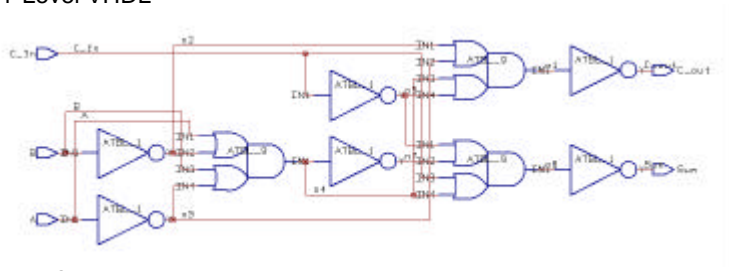

- 가 : 가
- (B3 Block Critical Path 가)
- B3 Behavioral View Model

VHDL

- System : Simulation Documentation
- Chip : Simulation, Synthesis Documentation
- Chip
 - IP(Intellectual Property) Model Re-Use 가
 - Synthesis가 가 VHDL Modeling 가




Full Adder	2가	VHDL
<p>✎ 1-Level VHDL</p> <pre> library IEEE; use IEEE.std_logic_1164.all; entity FULL_ADD is port (A : in std_logic; B : in std_logic; C_IN : in std_logic; C_OUT : out std_logic; SUM : out std_logic); end FULL_ADD; architecture RTL1 of FULL_ADD is signal S0 : std_logic; begin S0 <= A xor B; SUM <= S0 xor C_IN; C_OUT <= (A and B) or (S0 and C_IN); end RTL1; </pre>		<p>✎ VHDL</p> <pre> library IEEE; use IEEE.std_logic_1164.all; entity FULL_ADD is port (A, B, C_IN : in std_logic; SUM, C_OUT : out std_logic); end FULL_ADD; architecture RTL2 of FULL_ADD is signal S0,S1,S2 : std_logic; for u0,u1 : HA use entity work.HA(RTL); for u2 : OR2 use entity work.OR2(RTL); component HA port (A, B : in std_logic; SUM, CARRY : out std_logic); end component; component OR2 port (IN1, IN2 : in std_logic; OUT1 : out std_logic); end component; begin u0 : HA port map (X, Y, S0, S1); u1 : HA port map (S0, C_IN, SUM, S2); u2 : OR2 port map (S1, S2, C_OUT); end RTL2; </pre>
Univ. of Incheon System ASIC Design Lab.		VHDL ASIC NO.-27

Simulation Synthesis (1)	
<p>✎ Simulation</p>	<p>Waveform</p> 
<p>✎ 1-Level VHDL</p>	
<p>✎ LSI-10K Library : 3.0</p>	
Univ. of Incheon System ASIC Design Lab.	 VHDL ASIC NO.-28


Simulation Synthesis (2)

VHDL

Structural View Node

 

 Behavioral View Node (HA: Half Adder, OR2: 2-input OR)



LSI-10K Library : $1.5 * 2 + 0.5 = 3.5$

Optimization



VHDL

```


library IEEE;
use IEEE.std_logic_1164.all;
entity EX is
  port (A, B, C, D : in std_logic;
        Y1, Y2 : out std_logic);
end EX;
architecture RTL of EX is
begin
  process (A, B, C, D)
    variable TMP:
      std_logic_vector(3 downto 0);
  begin
    TMP := A & B & C & D;
    case TMP is
      when "0000" => Y1<='1'; Y2<='0';
      when "0001" => Y1<='1'; Y2<='0';
      when "0010" => Y1<='1'; Y2<='0';
      when "0011" => Y1<='1'; Y2<='0';
      when "0100" => Y1<='1'; Y2<='0';
      when "0101" => Y1<='1'; Y2<='0';
      when "0110" => Y1<='1'; Y2<='0';
      when "0111" => Y1<='1'; Y2<='0';
      when "1000" => Y1<='1'; Y2<='0';
      when "1001" => Y1<='0'; Y2<='1';
      when "1010" => Y1<='0'; Y2<='1';
      when "1011" => Y1<='1'; Y2<='1';
      when "1100" => Y1<='1'; Y2<='0';
      when "1101" => Y1<='1'; Y2<='0';
      when "1110" => Y1<='1'; Y2<='0';
      when "1111" => Y1<='1'; Y2<='0';
      when others => Y1<='1'; Y2<='0';
    end case;
  end process;
end RTL;
    
```



Target Library : LSI_10K


Area Area Design Constraint

 5-cells(Area : 7.0), Critical Path(2.38ns)



Timing Design Constraint

 
8-cells(Area : 15.0), Critical Path(0.84ns)



FPGA Fast Prototyping


FPGA Board

Reed-Solomon Decoder

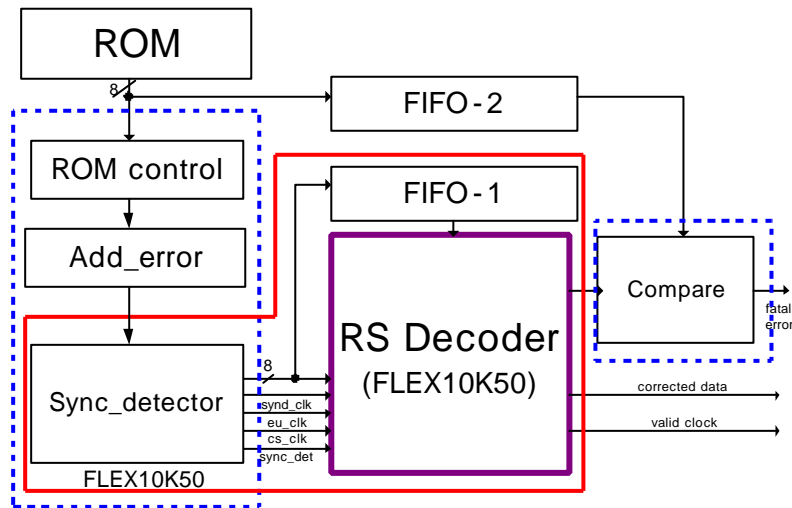

ASIC



Reed-Solomon Decoder Bonding Diagram

 

Chap. 2 VHDL

Character Set , Lexical Elements		Identifier	
<ul style="list-style-type: none"> ⌘ Character Sets <ul style="list-style-type: none"> ⌘ Upper-Case Letters ⌘ Lower-Case Letters ⌘ Special Characters ⌘ Space Character ⌘ Format Effectors ⌘ Lexical Elements <ul style="list-style-type: none"> ⌘ Delimiter <ul style="list-style-type: none"> ⌘ Single Character ⌘ Compound Character ⌘ Identifier <ul style="list-style-type: none"> ⌘ Reserved Identifier <ul style="list-style-type: none"> ⌘ 가 Identifier ⌘ Literal 	<ul style="list-style-type: none"> ⌘ VHDL-87 <ul style="list-style-type: none"> abs and assert buffer configuration downto entity function in library nand null others procedure record return subtype units when access architecture attribute bus constant else exit generate inout linkage new of out process register select then until while 	<ul style="list-style-type: none"> Reserved Word <ul style="list-style-type: none"> alias all array block body component disconnect end for guarded if label map mod nor not open or port range report signal transport type variable wait xor 	

VHDL-93 가 Reserved Word		Identifier	
<ul style="list-style-type: none"> ⌘ VHDL-93 가 Reserved Word <ul style="list-style-type: none"> group impure inertial literal postponed pure reject rol ror shared sla sll sra srl unaffected xnor ⌘ 가 Identifier <ul style="list-style-type: none"> ⌘ Alphabet ⌘ Alphabet ⌘ Alphabet, ⌘ ,_ ⌘ Alphabet ⌘ COUNT <ul style="list-style-type: none"> cout c_out AB2_5C VHSIC X1 FFT ⌘ Decoder <ul style="list-style-type: none"> A_B_C xyZ h333 STORE_NEXT_ITEM ⌘ 2CA <ul style="list-style-type: none"> My-name H\$B LOOP Decode_ N#3 			

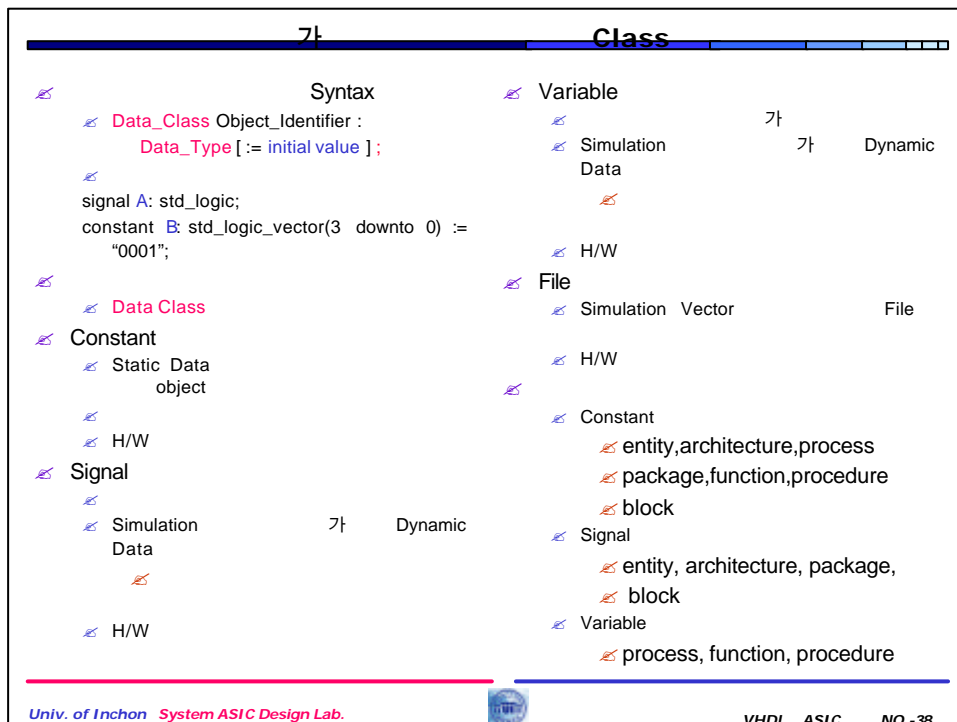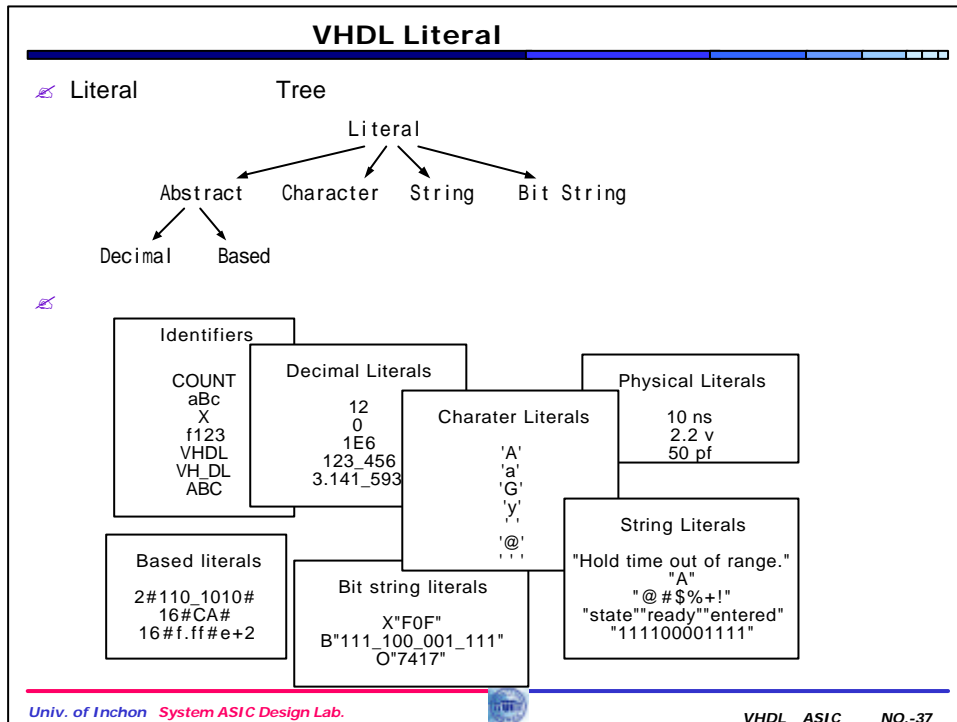

Data

<ul style="list-style-type: none"> ☞ Data <ul style="list-style-type: none"> ☞ Data Type <ul style="list-style-type: none"> ☞ Group, Package, Data Type ☞ VHDL 가 Data Type ☞ : ++ Type Synthesis ☞ Tool <ul style="list-style-type: none"> ☞ Scalar Data Types <ul style="list-style-type: none"> ☞ Enumeration Type, Numeric type, Physical Type** ☞ Composite Data Types <ul style="list-style-type: none"> ☞ Array Type, Record Type ☞ Access Data Type** ☞ File Data Type** ☞ Type package <ul style="list-style-type: none"> ☞ standard package <ul style="list-style-type: none"> ☞ 1987 ☞ std_logic_1164 ☞ 1993 	<ul style="list-style-type: none"> ☞ Standard Package <pre> package STANDARD is type BOOLEAN is (FALSE, TRUE); type BIT is ('0', '1'); type CHARACTER is (); type SEVERITY_LEVEL is (NOTE, WARNING, ERROR, FAILURE); type INTEGER is <i>implementation_defined</i>; type REAL is <i>implementation_defined</i>; type TIME is range <i>implementation_defined</i>; units fs: ps = 1000 fs; end units; subtype DELAY_LENGTH is TIME; function NOW return time; subtype NATURAL is integer range 0 to integer'high; subtype POSITIVE is integer range 1 to integer'high; type STRING is array(positive range <>) of character; type BIT_VECTOR is array(natural range <>) of bit; end STANDARD;</pre>
---	---

Univ. of Incheon System ASIC Design Lab. VHDL ASIC NO.-39

1993 Package Type

<ul style="list-style-type: none"> ☞ Std_logic_1164 Package <pre> package STD_LOGIC_1164 is type STD_ULOGIC is ('U', --Uninitialized 'X', --Forcing Unknown '0', --Forcing 0 '1', --Forcing 1 'Z', --High Impedance 'W', --Weak Unknown 'L', --Weak 0 'H', --Weak 1 '-' --Don't care); type STD_ULOGIC_VECTOR is array(natural range <>) of std_ulogic; function resolved(s: std_ulogic_vector) return std_ulogic; subtype STD_ULOGIC is resolved std_ulogic;</pre> 	<pre> type STD_LOGIC_VECTOR is array(natural range <>) of std_ulogic; subtype X01 is resolved std_ulogic range 'X' to '1'; subtype X01Z is resolved std_ulogic range 'X' to 'Z'; subtype UX01 is resolved std_ulogic range 'U' to '1'; subtype UX01Z is resolved std_ulogic range 'U' to 'Z'; function "and" (l: std_ulogic; r: std_ulogic) return std_ulogic; ; function "and" (l: std_ulogic_vector; r: std_ulogic_vector) return std_ulogic_vector; ; function is_X (s: std_ulogic) return boolean; end STD_LOGIC_1164;</pre>
---	--


Univ. of Incheon System ASIC Design Lab. VHDL ASIC NO.-40

가 Data Type (1)

Integer Data Type


- type **COUNTVALUE** is range 0 to 15;
- type **TWENTIES** is range 20 to 29;
- Synthesis tool bit

- Integer
- 0 ~ 15

 

Enumeration Data Type

 - FSM
- type **STATE_NAME** is (A, B, C, D);
- 2 가 (0)
- element 1 가



- type **STATE** is (S0, S1, S2);
- signal C_STATE, N_STATE : **STATE**;

가 Data Type (2)

8*5 Bit 2 Memory : -1

- Word Addressing Mode가 Memory
- 1
- subtype **WORD1** is
- std_logic_vector(4 downto 0);
- type **MEMORY1** is array(0 to 7) of
- WORD;

- 2
- type **WORD2** is array(4 downto 0) of
- std_logic;
- type **MEMORY2** is array(0 to 7) of
- WORD;

- 3
- type **MEMORY3** is array(0 to 7) of
- std_logic_vector(4 downto 0);

8*5 Bit 2 Memory : -2

- Bit Addressing Mode
- type **MEMORY4** is
- array(0 to 7, 4 downto 0) of std_logic;
- Bit-addressing Mode가 Memory 2

Composite Record Data Type

- type **FloatPointType** is
- record
- SIGN : std_logic;
- EXPONENT : unsigned(0 to 6);
- FRACTION : unsigned(24 downto 1);
- end record;

Composite Array Data Type

- type **unsigned** is array(natural range <>) of std_logic;
- type **unsigned_word** is array(natural range 7 downto 0) of std_logic;

Entity Declaration Unit

Entity Unit

Generic (static information: parameters)

Generic

Port (dynamic information)

Port

in
out
inout
buffer

Subtype constraint checks on generics
(values must belong to range) using passive process such as assertions
Dynamic checks on ports
(sequence of values must match arbitrary constraints - - set-up, hold)

Syntax

```
entity ENTITY_NAME is
  [ generic ( LIST_OF_GENERICS_AND_THEIR_TYPES ); ]
  [ port ( LIST_OF_PORTS_AND_THEIR_MODE ); ]
  [ DECLARATIONS ]
  [ begin
    { ENTITY_STATEMENT } ]
end [ ENTITY_NAME ] ;
```

Univ. of Incheon System ASIC Design Lab. VHDL ASIC NO.-43

Out Mode Buffer Mode

Out Mode

out mode

Buffer Mode

buffer mode

Buffer Mode

Buffer Mode

Buffer Mode


Buffer Mode

Out Mode

Univ. of Incheon System ASIC Design Lab. VHDL ASIC NO.-44

Entity Declaration Unit


✎ D Flip-Flop Entity Unit

 

```

-- 9-value Package
library IEEE; use IEEE.std_logic_1164.ALL;
-- Pin Name, Mode, Data Type
entity DFF is
    port (D : in std_logic;
          CLK : in std_logic;
          CLR : in std_logic;
          -- D, CLK, CLR : in std_logic;
          Q, QBAR : out std_logic);
end DFF;
    
```

✎ Generic Decoder Entity Unit

 

```

library IEEE; use IEEE.std_logic_1164.ALL;
entity GENERIC_DECODER is
    -- Static Information
    generic (SIZEIN, SIZEOUT : integer);
    -- Dynamic Pin Data
    port (EN: in std_logic;
          A: in std_logic_vector(SIZEIN-1
                                  downto 0);
          B : out std_logic_vector(SIZEOUT-1
                                    downto 0));
end GENERIC_DECODER;
    
```


Architecture Body Unit

✎ Syntax

```

architecture A_NAME of E_NAME is
    [ DECLARATIONS ]
begin
    {CONCURRENT_STATEMENT}
end [A_NAME] ;
    
```

✎

 

✎ Behavioral view

```

✎ Q='1'
✎ x='1' , Y Z가 '1'
    
```

✎ Data-flow view

```

✎ Boolean state equation
    
```

✎ Structural view

```

✎ and gate or gate
    
```

```

✎ and or gate Behavioral View
✎ Data-flow View
    
```

✎ Mixed view

```

✎ Behavioral View
✎ Data-flow View
✎ Structural View
    
```

```

✎ 가
    
```

Architecture Body Unit

Entity design unit

```
library IEEE; use IEEE.std_logic_1164.all;
entity EXAMPLE is
  port (X, Y, Z: in std_logic;
        Q: out std_logic);
end EXAMPLE;
```

Behavioral View

```
architecture RTL1 of EXAMPLE is
begin
  process (X, Y, Z)
  begin
    if X='1' then
      Q <= '1';
    elsif (Y='1' and Z='1') then
      Q <= '1';
    else
      Q <= '0';
    end if;
  end process;
end RTL1;
```

Data-flow View


```
architecture RTL2 of EXAMPLE is
begin
  Q <= X or (Y AND Z);
end RTL2;
```

Structural View

```
architecture RTL3 of EXAMPLE is
  component OR2
    port (I1, I2: in std_logic;
          O1: out std_logic);
  end component;
  component AND2
    port (I1, I2: in std_logic;
          O1: out std_logic);
  end component;
  for U0: OR2 use entity work.OR2(RTL);
  for U1: AND2 use entity work.AND2(RTL);
  signal S1: std_logic;
begin
  U0: OR2 port map (X, S1, Q);
  U1: AND2 port map (Y, Z, S1);
end RTL3;
```



Configuration

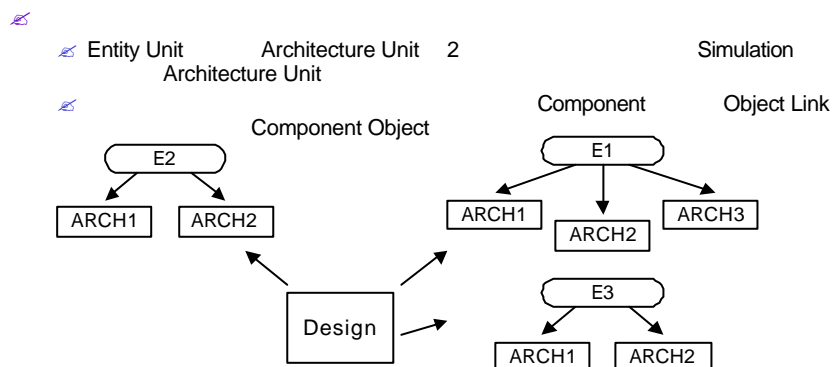

- Entity Unit EXAMPLE 37
- Simulation Entity Unit
- Architecture Unit
 - Configuration Specification
 - Configuration Unit
 - Configuration Declaration Unit



Configuration Specification :



- ✍ Architecture Unit Structural View
- ✍ component compile library entity unit
- ✍ architecture unit component binding
- ✍ 1-Level
- ✍ architecture unit
- ✍ Syntax
- ✍ for INSTANTIATION_LIST : COMPONENT_NAME
 - [use entity ENTITY_NAME { (ARCHITECTURE_NAME) }]
 - [generic map (GENERIC_ASSOCIATION_LIST)]
 - [port map (PORT_ASSOCIATION_LIST)] ;
- ✍
 - ✍ for U0 : NAND1, NAND2 use entity work.NAND_GATE(RTL);
 - ✍ 가
 - ✍ for U1 : INV1, INV2, INV3 use entity work.INVERTER;
 - ✍ for ALL : NOR use configuration LIB1.NOR_C;
 - ✍ NOR component 가 compile library LIB1
 - ✍ for others : NOT use entity work.NOT(RTL);



Configuration Declaration Unit :

- ✍ Behavioral View :
- ✍ configuration TOP of XDOWN is
- ✍ for BEHAVIORAL end for;
- ✍ end TOP;
- ✍ Structural View :
- ✍
 - ✍ design entity configuration
- ✍
- ✍ configuration FA_C of FA_E is
- ✍ for FA_A
- ✍ for u1,u2: HA use entity WORK.HA_E(HA_A) generic map (3 ns, 2 ns);
- ✍ for HA_A
- ✍ for u1: XOR2 use entity WORK.XOR2_E(XOR2_A) generic map (3 ns); end for;
- ✍ for u2: AND2 use entity WORK.AND2_E(AND2_A) generic map (2 ns); end for;
- ✍ end for;
- ✍ end for;
- ✍ for u3: OR2 use entity WORK.OR2_E(OR2_A) generic map (2 ns); end for;
- ✍ end for;
- ✍ end;
- ✍ Generate configuration declaration unit : generate



 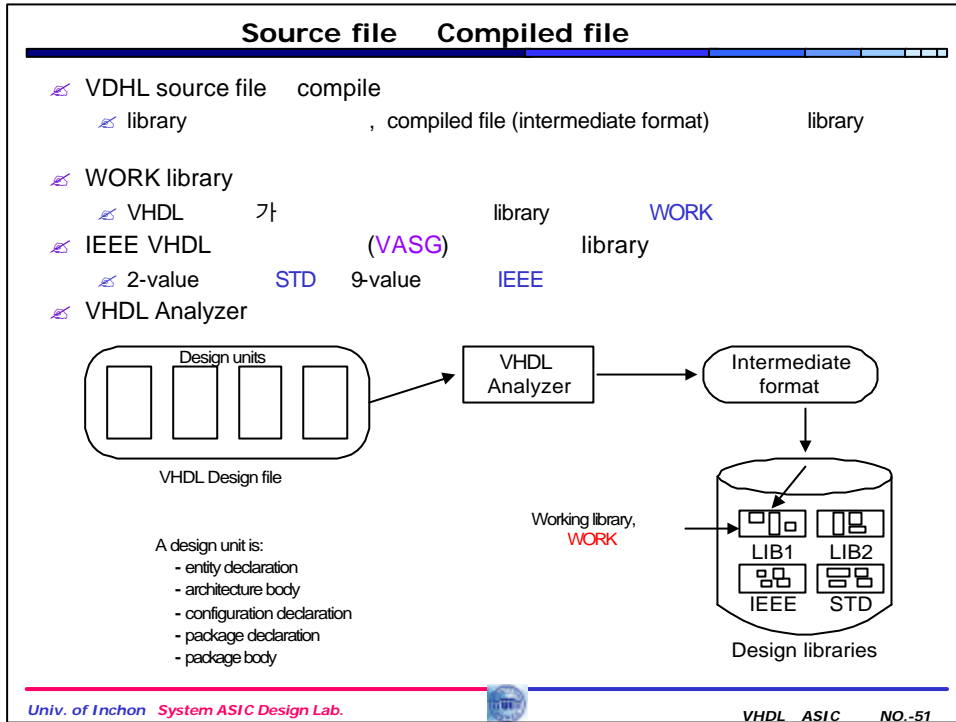

Library Visibility


```

Entity Unit
    architecture configuration unit
--library visibility
library IEEE; use IEEE.std_logic_1164.ALL; use IEEE.std_logic_unsigned.all;
--entity unit
entity ADD_SUB is
    port ( A, B      : in std_logic_vector(3 downto 0);
          SEL      : in std_logic;
          S        : out std_logic_vector(3 downto 0);
          CF, ZF   : out std_logic);
end ADD_SUB;

Package Declaration Unit
    package body unit
library IEEE; use IEEE.std_logic_1164.ALL;
use IEEE.std_logic_arith.all; use IEEE.std_logic_signed.all;
package PACK_MATCH is
    function COMP2C ( A: std_logic_vector) return std_logic_vector;
    function TWO_MUL ( A: std_logic_vector; B: std_logic) return std_logic_vector;
end PACK_MATCH;
    
```



Structural View

 

```

Structural View VHDL
Component
Architecture Unit
Component D.B.
Wire
Architecture Unit
Port Map
Component
Component
I/O Port
Formal Name: Pin Name
component HA
    port (A, B: in std_logic;
          C, D: out std_logic);
end component;

Component
Configuration
for U0: HA use entity work.HA(RTL);
Component
3가
Component Instantiation
Actual Name: Wire Name
Pin Wire
H/W
if for generate
Component Instantiation
Pin Wire 2가
Positional Association Mapping
Named Association Mappin
Wire Data Type
Signal
    
```



Component Instantiation

```


VHDL
library IEEE; use IEEE.std_logic_1164.all;
entity FA is
  port (A, B, CIN : in std_logic;
        SUM, COUT : out std_logic);
end FA;
--
architecture RTL of FA is
  component HA
    port (A, B : in std_logic;
          C, S : out std_logic);
  end component;
  component OR2
    port (A, B : in std_logic;
          Y : out std_logic);
  end component;
  for U0, U1: HA use entity work.HA(RTL);
  for U2: OR2 use entity work.OR2(RTL);
  signal S1, S2, S3 : std_logic;
begin
  --Positional Association Mapping
  U0 : HA port map (A, B, S1, S2);
  U1 : HA port map (CIN, S2, S3, SUM);
  U2 : OR2 port map (S1, S3, COUT);
  --Named Association Mapping
  --U0 : HA port map (A=>A, B=>B,
  --                  C=>S1, S=>S2);
  --U1 : HA port map (A=>CIN, B=>S1,
  --                  C=>S3, S=>SUM);
  --U2 : OR2 port map (A=>S1, B=>S3,
  --                  Y=>COUT);
end RTL;

```

Unconnected Port

Unconnected Port

- Pin Wire7 Port

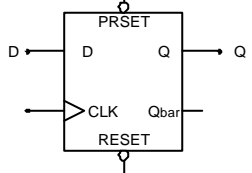

Unconnected Port

- Unconnected Output Port
- Unconnected Input Port

VHDL

- Unconnected Input Port
 - VCC '1'
 - GND '0'
- Unconnected Output Port
 - Reserved Identifier OPEN

```

Unconnected Port
architecture RTL of EX1 is
  component EX2
    port (CLK,PRESET,RESET,D:
          in std_logic;
          Q, QBAR : out std_logic);
  end component;
  for U1: EX2 use entity work.DSR(RTL);
  signal VCC : std_logic;
begin
  --VHDL-87
  VCC <= '1';
  U1 : EX2 port map (D => D,
                    CLK =>CLK, PRESET =>VCC,
                    RESET=>CLR, Q=>Q,
                    QBAR=>open);
  --VHDL-93
  --U1 : EX2 port map (D => D,
  --                  CLK=>CLK, PRESET =>'1',
  --                  RESET=>CLR, Q=>Q,
  --                  QBAR=>open);
end RTL;

```

Generic Map Command

\sphericalangle **Generic Behavioral**
 entity AND_GATE is
 generic (TDELAY : time := 10 ns;
 N : positive := 2);
 port (A : in std_logic_vector(N-1 downto 0);
 C : out std_logic);
 end AND_GATE;
 architecture RTL of AND_GATE is
 begin
 P0 : process (A)
 variable INT : std_logic;
 begin
 INT := '1';
 for I in (A'length-1) downto 0 loop
 if (A(I)='0') then
 INT := '0';
 end if;
 end loop;
 C <= INT after Tdelay;
 end process;
 end RTL;

\sphericalangle **Generic Map Structural**
 entity EX is
 port (D1, D2, D3, D4, D5 : in std_logic;
 Q1, Q2 : out std_logic);
 end EX;
 architecture RTL of EX is
 component AND_COMP
 generic (TDELAY : time; N : positive);
 port (A : in std_logic_vector(N-1 downto 0);
 C : out std_logic);
 end component;
 for all : AND_COMP use entity
 work.AND_GATE(RTL);
 begin
 U1: AND_COMP
 generic map (n=>2, TDELAY=>8 ns)
 port map (A(0)=>D1, A(1)=>D2, C=>Q1);
 U2: AND_COMP
 generic map (n=>3, TDELAY=>12 ns)
 port map (A(0)=>D3, A(1)=>D4,
 A(2)=>D5, C=>Q2);
 end RTL;




For Generate Structure View

\sphericalangle 4-Bit Ripple Carry Adder

\sphericalangle	Component	Symbol
Name	Formal Name	

\sphericalangle Component Instantiation

 

\sphericalangle Architecture Configuration Unit

```

architecture RTL1 of FA4 is
  -- FA Component
  signal TMP : std_logic_vector(4 downto 0);
begin
  TMP(0) <= '0';
  G: for I in 0 to 3 generate
    L : FA port map ( X(I), Y(I), TMP(I),
                   Z(I), TMP(I+1));
  end generate;
  COUT <= TMP(4);
end RTL1;
--
configuration CONF_FA4 of FA4 is
  for RTL
    for G
      for L: FA use entity work.FA(RTL); end for;
    end for;
  end for;
end CONF_FA4;

```

\sphericalangle Port Map
 \sphericalangle Configuration



If For..Generate	Structure View
<p>4-Bit Ripple Carry Adder</p> <p>Name Component Symbol</p> <p>Instantiation Component</p>	<p>Architecture Unit</p> <p>architecture RTL1 of FA4 is</p> <pre>-- FA, HA Component -- signal T : std_logic_vector(4 downto 1); begin G0: for I in 0 to 3 generate G1 : if I=0 generate L0 : HA port map (X(I),Y(I),Z(I),T(I+1)); end generate; G2 : if I>=1 and I<=3 generate L1 : FA port map (X(I),Y(I),T(I),Z(I),T(I+1)); end generate; end generate; COUT <= TMP(4); end RTL1;</pre>
<p>Univ. of Incheon System ASIC Design Lab.</p>	<p>VHDL ASIC NO.-59</p>

Generate	Configuration Declaration Unit
<p>Configuration Unit</p> <p>configuration CONF_FA4 of FA4 is</p> <p>for RTL1</p> <pre>for G0 for G1 for L0: HA use entity work.HA(RTL); end for; end for; for G2 for L1: FA use entity work.FA(RTL); end for; end for; end for;</pre> <p>end CONF_FA4;</p>	<p>Component</p> <p>component configuration</p> <p>architecture RTL of TB_FA4 is</p> <pre>signal X, Y: std_logic_vector(N-1 downto 0); signal Z: std_logic_vector(N-1 downto 0); signal COUT: std_logic; component FA4 generic(N: integer := 4); port (X: in std_logic_vector(N-1 downto 0); Y: in std_logic_vector(N-1 downto 0); Z: out std_logic_vector(N-1 downto 0); COUT: out std_logic); end component; for U0: FA4 use configuration work.CONF_FA4;</pre> <p>begin</p> <pre>U0: FA4 port map (X, Y, Z, COUT); X <= "0011", "1010" after 40 ns; Y <= "1000", "1110" after 20 ns;</pre> <p>end RTL;</p>
<p>Univ. of Incheon System ASIC Design Lab.</p>	<p>VHDL ASIC NO.-60</p>

H/W	Sensitivity Signal
<p>reset</p> <p>chip clock</p> <p>Spreading Code</p> <p>8-Bit Shift Register</p> <p>I</p> <p>Q</p> <p>I-Data</p> <p>Q-Data</p> <p>Sensitivity Signal</p> <p>Block</p> <p>Shift Register Block</p> <p>reset, chip clock</p> <p>XOR Gates Block</p> <p>I, Q Shift Register</p>	<p>Simulation</p> <p>Active State:</p> <p>Suspend State: Sensitivity Signal</p> <p>8-Bit Shift Register</p> <p>Reset='0' Falling Edge</p> <p>Chip Clock</p> <p>Shift</p> <p>XOR Gate Group</p> <p>Register, I, Q</p> <p>XOR</p> <p>VHDL</p> <p>3 Concurrent</p> <p>2 Concurrent</p> <p>1 Concurrent</p>
<p>Univ. of Incheon System ASIC Design Lab.</p>	<p>VHDL ASIC NO.-61</p>

VHDL	
<p>Behavioral View Concurrent</p> <ul style="list-style-type: none"> signal assignment statement <ul style="list-style-type: none"> basic signal assignment conditional signal assignment selected signal assignment process statement with many sequential statements concurrent subprogram call statement block statement <ul style="list-style-type: none"> basic block guarded block signal assignment concurrent assert statement <p>Structural View Concurrent</p> <ul style="list-style-type: none"> component instantiation statement Generate statement 	<p>Behavioral View</p> <ul style="list-style-type: none"> process function procedure subprogram wait statement Vector basic signal assignment statement variable assignment statement if statement case statement loop statements <ul style="list-style-type: none"> for..loop statement while loop statement infinite loop statement next statement, exit statement null statement sequential subprogram call statement sequential assert statement
<p>Univ. of Incheon System ASIC Design Lab.</p>	<p>VHDL ASIC NO.-62</p>


Data	Operator
<ul style="list-style-type: none"> ✎ Logical Operators <ul style="list-style-type: none"> ✎ not and or nand nor xor xnor(VHDL-93) ✎ Operand Type : std_logic, boolean ✎ Result Type : std_logic, boolean ✎ Relational Operators <ul style="list-style-type: none"> ✎ = /= < <= > >= ✎ Operand Type : any type ✎ Result Type: boolean ✎ Arithmetic Operators <ul style="list-style-type: none"> ✎ + - * / ** MOD REM ABS ✎ Operand Type : integer, real, physical ✎ Result Type: integer, real, physical ✎ Concatenation Operators : & <ul style="list-style-type: none"> ✎ Operand Type : array of any type ✎ Result Type : array of any type 	<ul style="list-style-type: none"> ✎ MOD REM <ul style="list-style-type: none"> ✎ $A = B*N + (A \text{ mod } B)$ (N:) ✎ $A = (A/B)*B + (A \text{ rem } B)$ ✎ A=10, B=3: A mod B = 1, A rem B = 1 ✎ A=-10, B=3: A mod B = 2, A rem B = -1 ✎ A=11, B=- 4: A mod B = -1, A rem B = 3 ✎ operator <ul style="list-style-type: none"> ✎ reset='0' or (clk='0' and clk'event) ✎ $A \leftarrow ((B \text{ nand } C) \text{ nand } D) \text{ nand } E;$ ✎ $A \leftarrow (B \text{ and } C) \text{ or } (D \text{ and } E)$




Predefined Type and Array Attributes																												
<ul style="list-style-type: none"> ✎ Attribute <ul style="list-style-type: none"> ✎ type attribute, array attribute, signal attribute, entity attribute ✎ Array Attribute <ul style="list-style-type: none"> ✎ Type 가 type COLOR is (RED, ORANGE, YELLOW, GREEN, BLUE, INDIGO, VIOLET); type STATE is (S0, S1, S2, S3, S4); type INDEXD is range 7 downto 0; 																												
<table border="0" style="width: 100%;"> <thead> <tr> <th style="text-align: left;">Signal Type Attribute</th> <th style="text-align: left;">Return Value</th> </tr> </thead> <tbody> <tr> <td>COLOR'pos(GREEN) = 3</td> <td>COLOR'val(3) = GREEN</td> </tr> <tr> <td>STATE'pos(S2) = 2</td> <td>STATE'val(0) = S0</td> </tr> <tr> <td>COLOR'left = RED</td> <td>STATE'left = S0</td> <td>STATE'right = S4</td> </tr> <tr> <td>COLOR'low = RED</td> <td>COLOR'high = VIORET</td> <td>STATE'high = S4</td> </tr> <tr> <td>COLOR'pred(GREEN) = YELLOW</td> <td>STATE'succ(S3) = S4</td> </tr> <tr> <td>COLOR'leftof(GREEN) = YELLOW</td> <td>STATE'rightof(S2) = S3</td> </tr> <tr> <td>INDEXD'left = 7</td> <td>INDEXD'right = 0</td> </tr> <tr> <td>INDEXD'low = 0</td> <td>INDEXD'high = 7</td> </tr> <tr> <td>INDEXD'pred(6) = 5</td> <td>INDEXD'leftof(6) = 7</td> </tr> <tr> <td>INDEXD'succ(6) = 7</td> <td>INDEXD'rightof(6) = 5</td> </tr> <tr> <td>INDEXD'range = 7 downto 0</td> <td>INDEXD'reverse_range = 0 to 7</td> </tr> <tr> <td>INDEXD'length = 8</td> <td></td> </tr> </tbody> </table>	Signal Type Attribute	Return Value	COLOR'pos(GREEN) = 3	COLOR'val(3) = GREEN	STATE'pos(S2) = 2	STATE'val(0) = S0	COLOR'left = RED	STATE'left = S0	STATE'right = S4	COLOR'low = RED	COLOR'high = VIORET	STATE'high = S4	COLOR'pred(GREEN) = YELLOW	STATE'succ(S3) = S4	COLOR'leftof(GREEN) = YELLOW	STATE'rightof(S2) = S3	INDEXD'left = 7	INDEXD'right = 0	INDEXD'low = 0	INDEXD'high = 7	INDEXD'pred(6) = 5	INDEXD'leftof(6) = 7	INDEXD'succ(6) = 7	INDEXD'rightof(6) = 5	INDEXD'range = 7 downto 0	INDEXD'reverse_range = 0 to 7	INDEXD'length = 8	
Signal Type Attribute	Return Value																											
COLOR'pos(GREEN) = 3	COLOR'val(3) = GREEN																											
STATE'pos(S2) = 2	STATE'val(0) = S0																											
COLOR'left = RED	STATE'left = S0	STATE'right = S4																										
COLOR'low = RED	COLOR'high = VIORET	STATE'high = S4																										
COLOR'pred(GREEN) = YELLOW	STATE'succ(S3) = S4																											
COLOR'leftof(GREEN) = YELLOW	STATE'rightof(S2) = S3																											
INDEXD'left = 7	INDEXD'right = 0																											
INDEXD'low = 0	INDEXD'high = 7																											
INDEXD'pred(6) = 5	INDEXD'leftof(6) = 7																											
INDEXD'succ(6) = 7	INDEXD'rightof(6) = 5																											
INDEXD'range = 7 downto 0	INDEXD'reverse_range = 0 to 7																											
INDEXD'length = 8																												

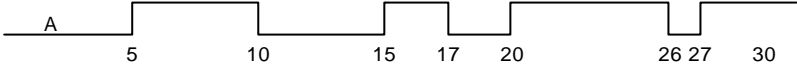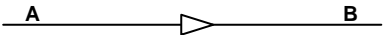
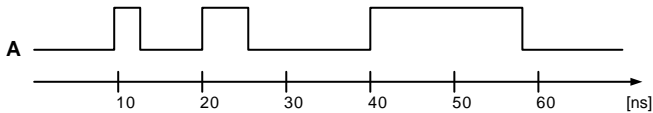
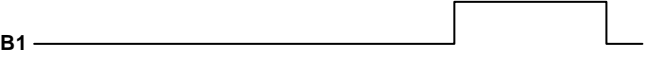

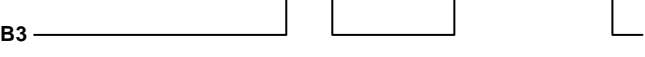



Delay Model (VHDL-87)

- Delay
 - Delay Selection
 - Inertial Delay : VHDL default delay
 - delay 가 noise
 - delay 가 .
 - Component delay
 - Transport Delay
 - 가 delay .
 - Interconnect delay modeling .
 - Internal Delay
 - Delta Delay : concurrent delay . event driven simulation
- Simulation : Plot
 - A 
 - B <= transport A after 3 ns;
 - C <= A after 3 ns;
 - D <= A;

Univ. of Incheon System ASIC Design Lab.  VHDL ASIC NO.-67

Delay Model (VHDL-93)


- VHDL-87 Inertial Delay Model
 - Reject Delay Model
 - 
 - A 
 - b1 <= inertial a after 10 ns;
 - b2 <= transport a after 10 ns;
 - b3 <= reject 4 ns inertial a after 10 ns;
 - B1 
 - B2 
 - B3 

Univ. of Incheon System ASIC Design Lab.  VHDL ASIC NO.-68

Delta Delay Model

VHDL Simulation Engine

Delay Model

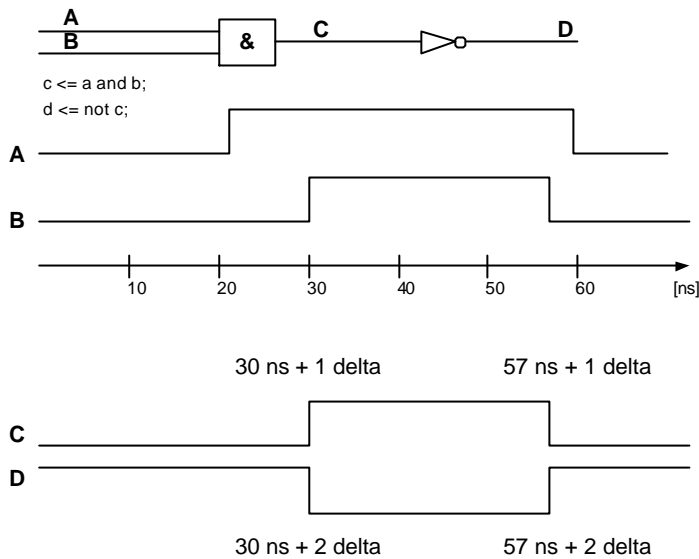


Basic Signal Assignment

Full-Adder Sensitivity Signal

Gate

Signal Assignment

 

Basic Signal Assignment Architecture Unit

architecture RTL of ADDER is

```

signal S0, S1 : std_logic;
begin
  -- gate signal assignment
  SUM <= S0 xor CIN;
  COUT <= S1 or (S0 and CIN);
  S0 <= A xor B;
  S1 <= A and B;
end RTL;
    
```

Aggregate : Target Signal Source

Assign

```

architecture RTL of EX is
  signal A : std_logic_vector( 4 downto 0);
  signal B : std_logic_vector( 4 downto 0);
begin
  A <= (others => '0');
  -- A <= "00000";
  -- A <= ('0', '0', '0', '0', '0');

  B <= (1=>C(2), 3=>C(1), others => D(0));
  -- B <= D(0)&C(1)&D(0)&C(2)&D(0);
end RTL;
    
```

Source Target Signal

Conditional Signal Assignment

Syntax

```
signal_identifier <= waveform_1 when condition_1 else
    waveform_2 when condition_2 else
    .....
    waveform_(N-1) when condition_(N-1) else
    waveform_N ;
```

D Type Flip-Flop VHDL Symbol


architecture A2 of DFF is

begin

```
Q <= '0' when CLR='0' else
    D when (CLK='0' and CLK'EVENT) else
    Q;
-- D when (CLK='0' and CLK'EVENT); Valid in VHDL-93
```

QBAR <= not Q;

end A2;

 

Data Selector Conditional Signal Assignment

```
MUXOUT <= I0 when (SEL='0') else
    I1; -- when (SEL='1') else 'X';
```



Selected Signal Assignment

Syntax

```
with expression select
signal_identifier <=
    waveform1 when expression_1,
    .....
    waveform(n-1) when expression(n-1),
    waveform(n) when others ;
```

2*1 MUX

```
library IEEE;
use IEEE.std_logic_1164.ALL;
entity MUX21 is
    port (SEL, A, B : in std_logic;
          C : out std_logic);
end MUX21;
architecture RTL of MUX21 is
begin
    with SEL select
        C <= A after 10 ns when '0',
            B after 10 ns when others;
end RTL;
```

Half-Adder

```
library IEEE;
use IEEE.std_logic_1164.ALL;
entity HA is
    port (A, B : in std_logic;
          SUM, COUT : out std_logic);
end HA;
architecture RTL of HA is
    signal TMP1, TMP2 :
        std_logic_vector(1 downto 0);
begin
    TMP1 <= A & B;
    with TMP1 select
        TMP2 <= "00" when "00",
            "01" when "01",
            "01" when "10",
            "10" when others;
    (COUT, SUM) <= TMP2;
end RTL;
```



Process

☞ Syntax
[Label :] **process** [(Sensitivity_Signals)]
-- declaration statements
begin
-- sequential activity statements
end process [Label] ;

☞ Sensitivity Signal

- ☞ Wait
- ☞ Simulation Signal
- ☞ 1
- ☞ Process Sensitivity Signal List
- ☞ Event가
- ☞ Event가
- ☞ Simulation
- ☞ H/W

☞ Sensitivity Signal

- ☞ 1 Wait
- ☞ Simulation Wait
- ☞ Wait
- ☞ Simulation
- ☞ Stimulus Vector

☞ Sensitivity Signal

- ☞ Half-Adder

```

process (A, B) process (A)
begin begin
SUM <= A xor B; SUM<=A xor B;
COUT <= A and B; COUT<=A and B;
end process; end process;

```

- ☞ Simulation ()
- ☞ Synthesis ()
- ☞

Univ. of Incheon System ASIC Design Lab. VHDL ASIC NO.-73

Signal Variable Assignment (1)

☞ Assignment : Target Identifier Object 2가

- ☞ Signal Assignment
 - ☞ [label:] signal_identifier <= [transport] expression [after expression];
- ☞ Variable Assignment
 - ☞ [label:] variable_identifier := value_expression;

☞ 2가 Assignment Code -1

```

process
variable num,sum:integer := 0;
begin
wait for 10 ns;
num := num + 1;
sum := sum + num;
end process;
--
process begin
wait for 10 ns;
num <= num + 1;
sum <= sum + num;
end process;

```

	<u>variable process</u>			<u>signal process</u>		
	<i>time</i>	<i>num</i>	<i>sum</i>	<i>time</i>	<i>num</i>	<i>sum</i>
	0	0	0	0	0	0
	10	1	1	10	0	0
	10+	1	1	10+	1	0
--	20	2	3	20	1	0
process begin	20+	2	3	20+	2	1
wait for 10 ns;	30	3	6	30	2	1
num <= num + 1;	30+	3	6	30+	3	3

Univ. of Incheon System ASIC Design Lab. VHDL ASIC NO.-74

Signal Variable Assignment

Signal Assignment

```

library IEEE; use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
entity EX_1 is end EX_1;
architecture RTL of EX_1 is
  signal A, B, C, D, X, Y:
    std_logic_vector(3 downto 0);
begin
  process (A, B, C, D)
  begin
    D <= A;
    X <= B + D;
    D <= C;
    Y <= B + D;
  end process;
  A <= "0001", "0010" after 10 ns,
    "0011" after 20 ns, "0100" after 30 ns;
  B <= "1000";
  C <= "0101", "0110" after 10 ns,
    "0111" after 20 ns, "1000" after 30 ns;
end RTL;
  
```

Variable Assignment


```

library IEEE; use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
entity EX_2 is end EX_2;
architecture RTL of EX_2 is
  signal A, B, C, X, Y:
    std_logic_vector(3 downto 0);
begin
  process (A, B, C)
  variable D: std_logic_vector(3 downto 0);
  begin
    D := A;
    X <= B + D;
    D := C;
    Y <= B + D;
  end process;
  A <= "0001", "0010" after 10 ns,
    "0011" after 20 ns, "0100" after 30 ns;
  B <= "1000";
  C <= "0101", "0110" after 10 ns,
    "0111" after 20 ns, "1000" after 30 ns;
end RTL;
  
```

Simulation Waveform


Signal Assignment

Simulation Waveform

 

Variable Assignment

Simulation Waveform

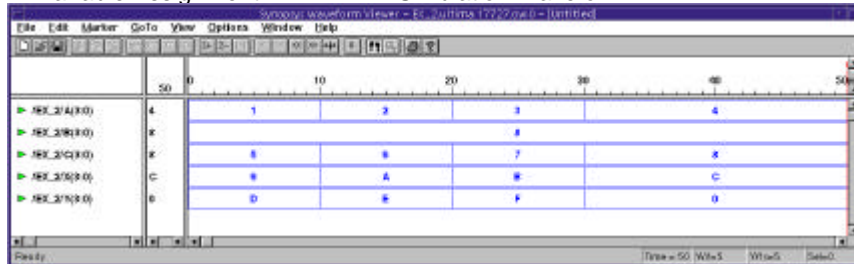

Wait

Syntax

`wait [on list] [until condition] [for time] ;`



`wait;`

Simulation Restart

`wait on A;`

Signal A Simulation

`wait until (CLK='0' and CLK'event);`

CLK Signal Falling Edge Simulation

`wait for 100 ns;`

100 ns Simulation

`wait until A='1' for 50 ns;`

50 ns A 가 A='1'

`wait on A until (C='1') for 50 ns;`

50 ns A 가 C='1'

Wait (가)

Synthesis Code : Clock wait Tool

wait until CLK Edge

Test Bench Modeling 가



Process

Process

```
process (A)
begin
  C1<=NOT A;
end process;
```

Simulation


```
process
begin
  C2<=NOT A;
  wait on A;
end process;
```

```
process
begin
  wait on A;
  C3<=NOT A;
end process;
```

```
process
begin
  wait until A='1';
  C4<=not A;
end process;
```

```
process
begin
  C5<=NOT A;
  wait until A='1' for 10 ns;
end process;
```

Simulation

 

Clock	Wait
<p>☞ Test Bench Modeling</p> <p>☞ 가 : CLK1, CLK2, CLK3, CLK4, CLK5, CLK6</p> <pre> process begin CLK1 <= not CLK1; wait for 25 ns; end process; -- process (CLK3) begin CLK3 <= not CLK3 after 25 ns; end process; -- process begin CLK5 <= '0'; wait for 20 ns; CLK5 <= '1'; wait for 30 ns; end process; </pre>	<p style="text-align: center;">VHDL</p> <p style="text-align: center;">'0' .</p> <pre> process begin CLK2 <= not CLK2 after 25 ns; wait on CLK2; end process; -- CLK4 <= not CLK4 after 25 ns; -- process begin if (now = 0 ns) then CLK6 <= '0'; wait for 100 ns; else CLK6 <= NOT CLK6; wait for 25 ns; end if; end process; </pre>
<p>☞ Quiz: Simulation</p>	
<p>Univ. of Incheon System ASIC Design Lab.</p>	<p>VHDL ASIC NO.-79</p>

If	
<p>☞ Syntax</p> <ul style="list-style-type: none"> ☞ if...then...end if; ☞ if... then...else...end if; ☞ if...then...elsif ...elsif ...else...end if; ☞ if...then...if...then.....end if....end if; <p>☞ Latch</p> <p>☞ IF</p> <p>☞ -1: 2*1 MUX</p> <pre> process (A, B, SEL) begin if SEL='0' then Y <= A; else Y <= B; end if; end process; </pre>	<p>☞ -2: 4*1 MUX</p> <pre> process (SEL, A, B, C, D) begin if SEL="00" then Y <= A; elsif SEL="01" then Y <= B; elsif SEL="10" then Y <= C; else Y <= D; end if; end process; </pre> <p>☞ -3: Latch</p> <pre> process (EN, D) begin if EN='1' THEN Q <= D; end if; end process; </pre>
<p>Univ. of Incheon System ASIC Design Lab.</p>	<p>VHDL ASIC NO.-80</p>

Case

Syntax

```

case expression is
  when condition_1 =>
    (sequential_statements;)
    ....
  when condition_(n-1) =>
    (sequential_statements;)
  when others =>
    (sequential_statements;)
end case ;
  
```

- when condition
- when Value =>
- when Value | Value | Value... =>
- when Value to Value =>
- when others =>

Truth Table

- 1 - Bit operator Variable
- Multi-Bits & expression

1-Bit Half-Adder

```

architecture RTL1 of EX is
  --signal TMP1 :
  --  std_logic_vector(1 downto 0);
begin
  --TMP1 <= A & B;
  --process (TMP1)
  process (A, B)
    variable TMP1, TMP2 :
      std_logic_vector(1 downto 0);
  begin
    TMP1 := A & B;
    case TMP1 is
      when "00" => TMP2 := "00";
      when "01" | "10" => TMP2 := "01";
      when others => TMP2 := "10";
    end case;
    (COUT, SUM) <= TMP2;
  end process;
end RTL;
  
```



For..Loop

Syntax

```

[Label:]
for loop_parameter in discrete_range loop
  --sequential statements
end loop [Label] ;
  
```

Range


- integer_expression to (downto)
- integer_expression array_attribute'range
- array_attribute'reverse_range

loop_parameter

- Signal Variable

For..Loop

Data-flow Graph
VHDL

 


- Signal Assignment
- Data-Flow
- For..Loop



For..Loop

 (1)


```
library IEEE; use IEEE.std_logic_1164.all;
package PACK is
  type RAM_TYPE is array(0 to 7) of
    std_logic_vector(7 downto 0);
end PACK;
library IEEE; use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
use work.PACK.all;
entity EX_3 is
  port (A: in RAM_TYPE;
        Y: out std_logic_vector(7 downto 0));
end EX_3;
architecture RTL of EX_3 is
begin
  process (A)
    variable SUM: std_logic_vector( 7 downto 0);
  begin
    SUM := (others => '0');
    for I in 0 to 7 loop
      SUM := SUM + A(I);
    end loop;
    Y <= SUM;
  end process;
end RTL;
```



For..Loop

 (2)

```
library IEEE; use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
use work.PACK.all;
entity EX_4 is
  port (A: in RAM_TYPE;
        Y: out std_logic_vector(7 downto 0));
end EX_4;
architecture RTL of EX_4 is
begin
  process (A)
    variable COUNT: integer;
    variable B: RAM_TYPE;
  begin
    COUNT := 8;
    for I in 0 to 7 loop
      B(I) := A(I);
    end loop;
    for LEVEL in 0 to 2 loop
      COUNT := COUNT / 2;
      for I in 0 to (COUNT-1) loop
        B(I) := B(I*2) + B(I*2+1);
      end loop;
    end loop;
    Y <= B(0);
  end process;
end RTL;
```



While..Loop

\leftarrow While..Loop Syntax
 [Label:] **while** condition **loop**
 --sequential statements
end loop [Label] ;
 \leftarrow 1 ~ N
 entity ADD_LOOP is
 port (N : in integer;
 SUM : out integer);
 end ADD_LOOP;
 architecture RTL of ADD_LOOP is
 begin
 process (N)
 variable TMP, I : integer;
 begin
 TMP := 0; I := 1;
 while (I <= N) **loop**
 TMP := TMP + I; I := I + 1;
 end loop;
 SUM <= TMP;
 end process;
 end RTL;

\leftarrow Infinite Loop
 process (N)
 variable TMP, I : integer;
 begin
 TMP := 0; I := 0;
 FIRST: loop
 I := I + 1;
 TMP := TMP + 1;
 exit when (I = N) ;
 end loop FIRST;
 end process;

\leftarrow Advanced Synthesis Tool
 가
 \leftarrow Behavioral Compiler



Next Exit

\leftarrow Next Syntax
 \leftarrow **next**;
 \leftarrow **next** loop_label ;
 \leftarrow **next when** boolean_expression ;
 \leftarrow **next** loop_label
 when boolean_expression ;
 \leftarrow
 LBL1 : process (S)
 variable TMP, J : integer := 0;
 begin
 TMP := 0; J := 0;
 A_LOOP: for I in 0 to 7 loop
 J := J + 1;
 if J > S then
 next A_LOOP;
 end if;
 TMP := TMP + 1;
 end loop;
 end process LBL1;

\leftarrow Exit Syntax
 \leftarrow **exit**;
 \leftarrow **exit** loop_label ;
 \leftarrow **exit when** boolean_expression ;
 \leftarrow **exit** loop_label
 when boolean_expression ;
 \leftarrow
 LBL2 : process (S)
 variable SUM, CNT : integer := 0;
 begin
 SUM:= 0; CNT:= 0;
 FIRST: loop
 CNT:=CNT+1; SUM:=SUM+CNT;
 exit when SUM > 100;
 end loop FIRST;
 --SECOND: loop
 -- CNT:=CNT+1; SUM:=SUM+CNT;
 -- if SUM > 100 then **exit**;
 --end loop SECOND;
 end process LBL2;



Block

Basic Block Statement

```

library IEEE; use IEEE.std_logic_1164.all;
entity BLK_FA is
  port ( A, B, C_IN: in std_logic;
        C_OUT, SUM: out std_logic);
end BLK_FA;
architecture RTL of BLK_FA is
  signal S0, S1, S2 : std_logic;
begin
  NAND_1: block begin
    S0 <= A xor B;
    S1 <= A and B;
  end block;
  NAND_2: block begin
    SUM <= S0 xor C_IN;
    S2 <= S0 and C_IN;
  end block;
  OR2: block begin
    C_OUT <= S1 or S2;
  end block;
end RTL;


```

Script File

```

read -f vhdl blk_fa.vhd
group -hdl_block nand_1
group -hdl_block nand_2
group -hdl_block or2
/* create_clock clk */
max_delay 0 -to all_outputs()
compile -map_effort high
create_schematic
write -f db
write -f edif -hierarchy -o blk_fa.edf

```

 

Guarded Block Statement

```

D_FF: block(clk='0' and clk'event)
begin
  Q <= guarded D;
end block;

```

Assert

(1)

Syntax


- assert condition ;
- assert condition report "message" ;
- assert condition severity level ;
- assert condition report "message" severity level ;

- Passive : HW
- Concurrent, Sequential Assert

D Flip-Flop Assert

- Setup Time Violation

Setup Time

 

Assert

```

library IEEE; use IEEE.std_logic_1164.all;
entity DFF_A_SR is
  generic (D_SETUP : time := 2 NS);
  port (SD_N, RD_N, CLK, DIN : in std_logic;
        Q, Q_N : out std_logic);
begin
  assert (SD_N='1' or RD_N='1')
    report "PRESET and CLEAR are both '0'" ;
  process (CLK, DIN)
    variable D_CHANGE : time := 0 ns;
    variable D_VALUE, CLK_VALUE : std_logic;
  begin
    if (D_VALUE /= DIN) then
      D_CHANGE := now; D_VALUE := DIN;
    end if;
    if (CLK_VALUE /= CLK) then
      CLK_VALUE := CLK;
      if (CLK='1') then
        assert (now - D_CHANGE >= D_SETUP)
          report "SETUP VIOLATION" ;
      end if;
    end if;
  end process;
end DFF_A_SR;

```

Assert

(2)

✍ Assert



Package

✍ Package

✍ Syntax

```
package package_name is
--exported_subprogram_declarations
--exported_constant_declarations
--exported_components
--exported_type_declarations
--attribute_declarations
--attribute_specifications
end [package_name] ;
package body package_name is
--exported_subprogram_bodies
--internal_subprogram_declarations
--internal_subprogram_bodies
--internal_constant_declarations
--internal_components
--internal_type_declarations
end [package_name] ;
```

✍ Package

```
package EX_PKG is
subtype INT8 is INTEGER range 0 to 255;
constant ZERO : INT8 := 0;
constant MAX : INT8 := 100;
procedure Increment (variable Count:
inout INT8);
end EX_PKG;
```

✍ Package

```
package body EX_PKG is
procedure Increment (variable Count:
inout INT8) is
begin
if (Count >= MAX) then
Count := Zero;
else
Count := Count + 1;
end if;
end Increment;
end EX_PKG;
```



Predefined Package

<ul style="list-style-type: none"> Predefined Packages <ul style="list-style-type: none"> Group Package. Library Name : STD Package Name <ul style="list-style-type: none"> standard textio textio package visibility Library Name : IEEE Package Name <ul style="list-style-type: none"> std_logic_1164 std_logic_textio Visibility Synopsys Package. <ul style="list-style-type: none"> Library Name : IEEE Package Name <ul style="list-style-type: none"> std_logic_unsigned std_logic_signed std_logic_arith 	<ul style="list-style-type: none"> Package <ul style="list-style-type: none"> \$/synopsys/packages/IEEE/src/*.vhd std_logic_1164.vhd std_logic_arith.vhd std_logic_signed.vhd std_logic_unsigned.vhd std_logic_textio.vhd
--	---

Unsigned Data

<ul style="list-style-type: none"> Data Type: std_logic_vector Package: std_logic_unsigned <p>VHDL</p> <pre> library ieee; use ieee.std_logic_1164.all; use ieee.std_logic_unsigned.all; entity TB_UNSIGNED is end TB_UNSIGNED; architecture RTL of TB_UNSIGNED is signal s1, s2 : std_logic_vector(3 downto 0); signal a, b : std_logic_vector(4 downto 0); signal c, d : std_logic_vector(7 downto 0); begin process begin s1 <= "0011"; s2 <= "0101"; wait for 50 ns; s1 <= "1101"; s2 <= "0101"; wait for 50 ns; s1 <= "1101"; s2 <= "1011"; wait for 50 ns; s1 <= "0011"; s2 <= "1011"; wait for 50 ns; end process; a <= (0&s1) + s2; b <= (0&s1) - s2; c <= s1 * s2; d <= s1 * "1000"; end RTL; </pre>	<ul style="list-style-type: none"> Data Type: unsigned Package: std_logic_arith <p>VHDL</p> <pre> library ieee; use ieee.std_logic_1164.all; use ieee.std_logic_arith.all; entity TB_ARITH_UNSIGNED is end TB_ARITH_UNSIGNED; architecture RTL of TB_ARITH_UNSIGNED is signal s1, s2 : unsigned(3 downto 0); signal a, b : unsigned(4 downto 0); signal c : unsigned(7 downto 0); begin process begin s1 <= "0011"; s2 <= "0101"; wait for 50 ns; s1 <= "1101"; s2 <= "0101"; wait for 50 ns; s1 <= "1101"; s2 <= "1011"; wait for 50 ns; s1 <= "0011"; s2 <= "1011"; wait for 50 ns; end process; a <= (0&s1) + s2; b <= (0&s1) - s2; c <= s1 * s2; end RTL; </pre>
---	---

Unsigned Data Simulation

✎ `std_logic_vector` `std_logic_unsigned` package Simulation

✎ `unsigned` `std_logic_arith` package simulation

Univ. of Incheon System ASIC Design Lab. VHDL ASIC NO.-93

Signed Data

✎ Data Type: `std_logic_vector`
✎ Package: `std_logic_signed`

✎ VHDL
 library ieee; use ieee.std_logic_1164.all;
 use **ieee.std_logic_signed.all;**
 entity TB_SIGNED is end TB_SIGNED;
 architecture RTL of TB_SIGNED is
 signal s1, s2 : std_logic_vector(3 downto 0);
 signal a,b : std_logic_vector(4 downto 0);
 signal c, d : std_logic_vector(7 downto 0);
 begin
 process
 begin
 s1 <= "0011"; s2 <= "0101"; wait for 50 ns;
 s1 <= "1101"; s2 <= "0101"; wait for 50 ns;
 s1 <= "1101"; s2 <= "1011"; wait for 50 ns;
 s1 <= "0011"; s2 <= "1011"; wait for 50 ns;
 end process;
 a <= (s1(3)&s1) + (s2(3)&s2);
 b <= (s1(3)&s1) - (s2(3)&s2);
 c <= s1 * s2; d <= s1 * "1000";
 end RTL;

✎ Data Type: `signed`
✎ Package: `std_logic_arith`

✎ VHDL
 library ieee; use ieee.std_logic_1164.all;
 use ieee.std_logic_arith.all;
 entity TB_ARITH_SIGNED is
 end TB_ARITH_SIGNED;
 architecture RTL of TB_ARITH_SIGNED is
 signal s1, s2 : signed(3 downto 0);
 signal a, b : signed(4 downto 0);
 signal c : signed(7 downto 0);
 begin
 process
 begin
 s1 <= "0011"; s2 <= "0101"; wait for 50 ns;
 s1 <= "1101"; s2 <= "0101"; wait for 50 ns;
 s1 <= "1101"; s2 <= "1011"; wait for 50 ns;
 s1 <= "0011"; s2 <= "1011"; wait for 50 ns;
 end process;
 a <= (s1(3)&s1) + (s2(3)&s2);
 b <= (s1(3)&s1) - (s2(3)&s2);
 c <= s1 * s2;
 end RTL;


Univ. of Incheon System ASIC Design Lab. VHDL ASIC NO.-94

Signed Data Simulation

std_logic_vector std_logic_signed package simulation



 signed std_logic_arith package simulation



Subprogram Function Subprogram

- | | |
|---|---|
| <ul style="list-style-type: none"> Subprogram <ul style="list-style-type: none"> Function Procedure Subprogram <ul style="list-style-type: none"> Package Package Architecture Process Function Syntax <ul style="list-style-type: none"> Package <pre>function name (formal_parameter_list) return data_type is Package function name (formal_parameter_list) return data_type is -- declarative statements begin -- sequential statements -- including return expression end name ;</pre> | <ul style="list-style-type: none"> Parameter <ul style="list-style-type: none"> Data Mode <ul style="list-style-type: none"> in Data Object <ul style="list-style-type: none"> constant signal constant Formal Name Actual Name <ul style="list-style-type: none"> signal :signal 가 constant : signal,constant,variable 가 Function Visibility <ul style="list-style-type: none"> Package 가 Package Body 가 Package Body 가 Architecture 가 Architecture 가 Process 가 Process 가 |
|---|---|

Function Subprogram

Function Subprogram

```

package MYPACK is
  function MAX (A, B: in std_logic_vector)
    return std_logic_vector;
  function EQUAL (A, B : in std_logic_vector)
    return boolean;
end;
package body MYPACK is
  function MAX (A, B: in std_logic_vector)
    return std_logic_vector is
  begin
    if A > B then
      return (A);
    else
      return (B);
    end if;
  end MAX ;
  function EQUAUL(A, B : in std_logic_vector)
    return boolean is
  begin
    return (A=B);
  end EQUAL;
end MYPACK;

```

Function Subprogram

```

library IEEE; use IEEE.std_logic_1164.all;
use work.MYPACK.all;
entity EX is
  port (D1, D2: in
         std_logic_vector(3 downto 0);
        DATA1, DATA2: in
         std_logic_vector(7 downto 0);
        Q: out std_logic_vector(3 downto 0);
        DATA_OUT: out boolean);
end EX;
architecture RTL of EX is
begin
  Q <= MAX(d1, d2);
  --Concurrent function call
  process (DATA1, DATA2)
  begin
    DATA_OUT <= EQUAL(DATA1, DATA2);
    --Sequential function call
  end process;
end RTL;

```

Procedure Subprogram

Procedure Syntax

```

Package
procedure name (formal_parameter_list) ;
Package
procedure name (formal_parameter_list) is
-- declarative statements
begin
-- sequential statements
end name ;
Parameter
  Data Mode
    in, out, inout 가
  Data Class
    Mode가 in ,
    constant, signal, variable 가
    Mode가 in ,
    constant

```

```

Mode가 inout out ,
variable, signal 가
Mode가 inout out ,
variable
Formal Name Actual Name
signal :signal 가
variable : variable 가
constant :
signal,constant,variable 가
Procedure Visibility
Package
Package 가
Package Body
가 Package Body
Architecture
가 Architecture
가
Process
Process 가

```

Procedure Subprogram (1)

```

✎ Procedure
package MYPACK is
  procedure COMPUTE (A, B: in integer;
    MEAN, MAX: out integer);
end MYPACK;
package body MYPACK is
  procedure COMPUTE (A, B: in integer;
    MEAN, MAX: out integer) is
  begin
    MEAN := (A+B)/2;
    if A > B then
      MAX := A;
    else
      MAX := B;
    end if;
  end COMPUTE;
end MYPACK;
  
```

```

✎ Procedure
use work.MYPACK.all;
entity EX is
  port (D1, D2, D3, D4: in integer;
    Q1, Q2, Q3, Q4: out integer);
architecture RTL1 of EX is
begin
  COMPUTE(D1, D2, Q1, Q2);
  --           , Q1, Q2 not variables
  --Concurrent procedure call
  process(D3, D4)
    variable A, B: integer;
  begin
    COMPUTE(D3, D4, A, B);
    --           , A and B variables
    --Sequential procedure call
    Q3 <= A;
    Q4 <= B;
  end process;
end RTL1;
  
```



Procedure Subprogram (2)

```

✎ Procedure
package MYPACK is
  procedure COMPUTE (A, B: in integer;
    signal MEAN, MAX: out integer);
end MYPACK;
package body MYPACK is
  procedure COMPUTE (A, B: in integer;
    signal MEAN, MAX: out integer) is
  begin
    MEAN <= (A+B)/2;
    if A > B then
      MAX <= A;
    else
      MAX <= B;
    end if;
  end COMPUTE;
end MYPACK;
  
```

```

✎ Procedure
use work.MYPACK.all;
entity EX is
  port (D1, D2, D3, D4: in integer;
    Q1, Q2, Q3, Q4: out integer);
architecture RTL2 of EX is
begin
  COMPUTE(D1, D2, Q1, Q2);
  --           , Q1 and Q2 signals
  --Concurrent procedure call
  process(D3, D4)
  begin
    COMPUTE(D3, D4, Q3, Q4);
    --           , Q3 and Q4 signals
    --Sequential procedure call
  end process;
end RTL2;
  
```



Procedure Subprogram (3)

```

library IEEE; use IEEE.std_logic_1164.ALL;
package EXAMPLE is
  procedure RCA (A, B : in std_logic_vector;
    CIN : in std_logic; SUM : out std_logic_vector;
    COUT : out std_logic);
end EXAMPLE;
package body EXAMPLE is
  function XOR3 (A, B, C : in std_logic) return
    std_logic is
  begin
    return (A xor B xor C);
  end XOR3;
  procedure RCA (A, B : in std_logic_vector;
    CIN : in std_logic; SUM : out std_logic_vector;
    COUT : out std_logic) is variable C :
    std_logic_vector(A'high-A'low+1 downto 0);
  begin
    C(0) := CIN;
    for I in 0 to (A'high-A'low) loop
      SUM(I+SUM'low) :=
        XOR3(A(I+A'low), B(I+B'low), C(I));
      C(I+1) := (A(I+A'low) and (I+B'low))
        or (C(I) and (A(I+A'low) or B(I+B'low)));
    end loop;
    COUT := C(C'high);
  end RCA;
end EXAMPLE;
  
```

```

library IEEE; use IEEE.std_logic_1164.ALL;
use work.EXAMPLE.all;
entity ADDER_TEST is
  port ( A, B: in
    std_logic_vector(15 downto 0);
    CIN : in std_logic;
    SUM : out
    std_logic_vector(15 downto 0);
    COUT : out std_logic);
end ADDER_TEST;
architecture RTL of ADDER_TEST is
begin
  process (A,B,CIN)
    variable TMP_SUM:
      std_logic_vector(SUM'range);
    variable TMP_COUT : std_logic;
  begin
    RCA(A, B, CIN, TMP_SUM, TMP_COUT);
    SUM <= TMP_SUM;
    COUT <= TMP_COUT;
  end process;
end RTL;
  
```



Operator Overload

<pre> type 가 type function Function " " " " " " Synopsis Vendor가 Package function "+" (L: std_logic_vector, R: std_logic_vector) return std_logic_vector; function "+" (L: std_logic_vector, R: integer) return std_logic_vector; </pre>	<pre> VHDL Compiler Compile VHDL Code + Operator Compiler Operand Data Type Function Type Function Function Algorithm Function Error Message Function Algorithm C <= A + B A, B가 std_logic_vector A std_logic_vector , B integer Function Name </pre>
--	--



Subprogram Overload



<pre> -- Subprogram -- , Formal Parameter -- Return Value Data Type -- Subprogram -- library IEEE; use IEEE.std_logic_1164.ALL; use IEEE.std_logic_arith.all; use IEEE.std_logic_unsigned.all; package EXAMPLE is function CONV_2COMP (A : std_logic_vector; K : integer) return std_logic_vector; function CONV_2COMP (A : integer; K : integer) return std_logic_vector; end EXAMPLE;</pre>	<pre> package body EXAMPLE is function CONV_2COMP (A : std_logic_vector; K : integer) return std_logic_vector is begin return (not (A(K-1) downto 0)+1); end; -- function CONV_2COMP (A : integer; K : integer) return std_logic_vector is begin return (not conv_std_logic_vector(A,K)+1); end; end EXAMPLE;</pre>
--	---

-- VHDL Compiler
 -- B <= CONV_2COMP(A, 8);
 -- A7↑ std_logic_vector
 -- A7↑ integer



Chap 3. Digital System VHDL Modeling

Digital System RTL

  

Digital System VHDL Modeling Template

H/W Model VHDL Modeling

- Entity + Architecture
- Entity Unit
 - Visibility
 - 9-value Visibility
 - Arithmetic Operator Visibility
 - Package
 - Visibility
 - Block Diagram
 - Generic, Port Data
 - Data Identifier, Mode, Type

Architecture Unit

-
-
-



가

Basic Modeling Template

```

library IEEE; use IEEE.std_logic_1164.ALL;
entity name is
  port (
    end name;
  architecture architecture_name of name is
    ( : signal);
  begin
    -- 가
    sync : process (clock, reset )
    begin
      VHDL statements for state elements
    end process sync;
    -- ( )
    --
    comb : process (
      ( : variable)
    begin
      end process comb;
    end architecture_name;
  
```




4-Bit Up-Counter

VHDL Modeling

Counter Table

RST	CLK	ENB	LOADB	DOUT
0	X	X	X	"0000"
1		1	0	DIN
1		1	1	DOUT+1

Block Diagram

 

VHDL

```

library IEEE; use IEEE.std_logic_1164.ALL;
use IEEE.std_logic_unsigned.all;
entity COUNTER is
port ( RST,CLK,LOADB,ENB: in std_logic;
      DIN : in std_logic_vector(3 downto 0);
      DOUT : out std_logic_vector(3 downto 0));
end COUNTER;
    
```

```

architecture RTL of COUNTER is
signal T1,T2: std_logic_vector(3 downto 0);
begin
A: process (RST, CLK) begin
if RST = '0' then
T1 <= (others => '0');
elsif CLK'event and CLK = '1' then
if ENB = '1' then
T1 <= T2;
end if;
end if;
end process;
--
B: process (LOADB, DIN, T1) begin
if LOADB='0' then
T2 <= DIN;
else
T2 <= T1 + 1;
end if;
end process;
--
DOUT <= T1;
end RTL;
    
```

Gate-Level


Boolean Equation

Shift Data

Arithmetic Logic

3-state Buffer

가

 

Gate Logic Operator

Wire Signal

Signal Assign

```

library IEEE; use IEEE.std_logic_1164.ALL;
    
```

```

entity ADDER is
port (A, B, CIN : in std_logic;
      SUM, COUT : out std_logic);
end ADDER;
    
```

```

architecture RTL1 of ADDER is
    
```

```

-- Wire Signal
signal S0, S1, S2 : std_logic;
begin
    
```

```

-- Gate Logical Operator
    
```

```

S0 <= A xor B;
S1 <= A and B;
SUM <= S0 xor CIN;
S2 <= S0 and CIN;
COUT <= S1 or S2;
end RTL1;
    
```

Boolean Equation		VHDL	
가	Equation	Multi-Bit	Entity Unit
	$sum = \bar{a}b\bar{c}_{in} + a\bar{b}\bar{c}_{in} + \bar{a}b\bar{c}_{in} + abc_{in}$		entity MULTIBIT is port (A,B,C : IN std_logic_vector(3 DOWNT0 0); Z: OUT std_logic_vector(3 DOWNT0 0)); end MULTIBIT;
	$cout = \bar{a}b\bar{c}_{in} + \bar{a}bc_{in} + a\bar{b}c_{in} + abc_{in}$	2가	Architecture Unit
	Boolean Equation Data Flow		architecture RTL2 of MULTIBIT is begin --Multi-Bit Z <= A or (B nand C); end RTL2;
	Signal Assign		-- architecture RTL1 of MULTIBIT is begin -- Bit Equation Z(3) <= A(3) nor (B(3) nand C(3)); Z(2) <= A(2) nor (B(2) nand C(2)); Z(1) <= A(1) nor (B(1) nand C(1)); Z(0) <= A(0) nor (B(0) nand C(0)); end RTL1;
	architecture RTL2 of ADDER is begin SUM <= (not A and not B and Cin) or (not A and B and not Cin) or (A and B and not Cin) or (A and B and Cin); COUT <= (not A and B and Cin) or (A and not B and Cin) or (A and B and not Cin) or (A and B and C); end RTL2;		

Truth Table		VHDL																																														
1-Bit 가	Truth Table	Architecture Unit																																														
	<table border="1"> <thead> <tr> <th>a</th> <th>b</th> <th>cin</th> <th>sum</th> <th>cout</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>0</td><td>1</td><td>1</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td><td>1</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	a	b	cin	sum	cout	0	0	0	0	0	0	0	1	1	0	0	1	0	1	0	0	1	1	0	1	1	0	0	1	0	1	0	1	0	1	1	1	0	0	1	1	1	1	1	1	architecture RTL2 of ADDER is begin process (A, B, CIN) variable TMP : std_logic_vector(2 downto 0); begin -- variable TMP := A & B & CIN; case TMP is when "000" => SUM <='0'; COUT <='0'; when "001" "010" "100" => SUM <='1'; COUT <='0'; when "011" "101" "110" => SUM <='0'; COUT <='1'; when others => SUM <='1'; COUT <='1'; end case; end process; end RTL2;	
a	b	cin	sum	cout																																												
0	0	0	0	0																																												
0	0	1	1	0																																												
0	1	0	1	0																																												
0	1	1	0	1																																												
1	0	0	1	0																																												
1	0	1	0	1																																												
1	1	0	0	1																																												
1	1	1	1	1																																												
1 - Bit	Variable	&																																														
	가	Case																																														
	Signal Assign																																															
	Variable Assign																																															

VHDL

4*2 Priority Encoder

a	b	c	d	enc out
-	-	-	0	00
-	-	0	1	01
-	0	1	1	10
0	1	1	1	11

```

Conditional Signal Assign
Process IF
Conditional Signal Assign
architecture RTL1 of PRIO_ENC is
begin
  ENC_OUT <= "00" when D = '0' else
    "01" when C = '0' else
    "10" when B = '0' else
    "11";
end RTL1;

```

```

Process IF
가
1
architecture RTL2 of PRIO_ENC is
begin
  process (A,B,C,D)
  begin
    if D='0' then
      ENC_OUT <= "00";
    elsif C='0' then
      ENC_OUT <= "01";
    elsif B='0' then
      ENC_OUT <= "10";
    else
      ENC_OUT <= "11";
    end if;
  end process;
end RTL2;

```



(1)

Enable 4*1 MUX

ENABLE	SEL	Y
0	00	I0
0	01	I1
0	10	I2
0	11	I3
1	--	"0000"

```

Process Case
process(SEL,ENABLE,I0,I1,I2,I3) begin
  if ENABLE='0' then
    case SEL is
      when "00" => Y <= I0;
      when "01" => Y <= I1;
      when "10" => Y <= I2;
      when others => Y <= I3;
    end case;
  else
    Y <= "0000";
  end if;
end process;

```

```

Selected Signal Assign
architecture RTL2 of MUX41 is
  signal TMP : std_logic_vector(1 downto 0);
begin
  with SEL select
    TMP <= I0 when "00",
      I1 when "01",
      I2 when "10",
      I3 when others;
  with ENABLE select
    Y <= TMP when '0',
      "0000" when others;
end RTL2;

```

```

MUX
MUX Component
, Structural Modeling
process
case
, Tool

```



Enable 2*4 DEC

Enable G	DATA	Y
0	00	"1110"
0	01	"1101"
0	10	"1011"
0	11	"0111"
1	--	"1111"

```

Process
process(G,DATA) begin
  if G='0' then
    case DATA is
      when "00" => Y <= "1110";
      when "01" => Y <= "1101";
      when "10" => Y <= "1011";
      when others => Y <= "0111";
    end case;
  else
    Y <= "1111";
  end if;
end process;


```

Selected Signal Assign
architecture RTL2 of EDECODER is
signal TMP : std_logic_vector(2 downto 0);
begin
TMP <= G & DATA;
with TMP select
Y <= "1110" when "000",
"1101" when "001",
"1011" when "010",
"0111" when "011",
"1111" when others;


end RTL2;

BCD-to-7 Segment Decoder

Don't Care
VHDL

 

Shift Data VHDL

 

Basic Signal Assign & Operator
& Operator : Shift Rotate
-- DATA4(7 downto 3) <= DATA1(4 downto 0);
-- DATA4(2 downto 0) <= DATA1(7 downto 5);
DATA4 <= DATA1(4 downto 0) & DATA1(7 downto 5);
-- DATA5(7 downto 5) <= "000";
-- DATA5(4 downto 0) <= DATA2(7 downto 3);
DATA5 <= "000" & DATA2(7 downto 3);
-- DATA6(7) <= DATA3(7);
-- DATA6(6 downto 3) <= DATA3(3 downto 0);
-- DATA6(2 downto 0) <= "000";
DATA6 <= DATA3(7) & DATA3(3 downto 0) & "000";


Arithmetic	VHDL																
<p>8가 ALU</p> <table border="1" style="margin-left: 20px; border-collapse: collapse;"> <tr><td>000</td><td>op1 + op2</td></tr> <tr><td>001</td><td>op1 - 1</td></tr> <tr><td>010</td><td>op1 - op2</td></tr> <tr><td>011</td><td>op1 + 1</td></tr> <tr><td>100</td><td>op1 and op2</td></tr> <tr><td>101</td><td>op1 or op2</td></tr> <tr><td>110</td><td>not op1</td></tr> <tr><td>111</td><td>op1</td></tr> </table> <p>Entity Unit</p> <pre> library IEEE; use IEEE.std_logic_1164.ALL; use IEEE.std_logic_unsigned.all; entity SIM_ALU is port (OP1,OP2:in std_logic_vector(7 downto 0); CIN : in std_logic; SEL : in std_logic_vector(2 downto 0); ALU_OUT : out std_logic_vector(7 downto 0); ZERO_FLAG : out std_logic); end SIM_ALU; </pre>	000	op1 + op2	001	op1 - 1	010	op1 - op2	011	op1 + 1	100	op1 and op2	101	op1 or op2	110	not op1	111	op1	<p>Case</p> <pre> architecture RTL of SIM_ALU is begin process (OP1, OP2, CIN, SEL) variable TMP:std_logic_vector(7 downto 0); begin case SEL is when '000'=>TMP:= OP1+OP2+CIN; when '001'=>TMP:= OP1-1; when '010'=>TMP:= OP1-OP2+CIN; when '011'=>TMP:= OP1+1; when '100'=>TMP:= OP1 and OP2; when '101'=>TMP:= OP1 or OP2; when '110' =>TMP:= not OP1; when others =>TMP:= OP1; end case; ALU_OUT <= TMP; if TMP=0 then ZERO_FLAG <= '1'; else ZERO_FLAG <= '0'; end if; end process; end RTL; </pre>
000	op1 + op2																
001	op1 - 1																
010	op1 - op2																
011	op1 + 1																
100	op1 and op2																
101	op1 or op2																
110	not op1																
111	op1																
<p>Univ. of Incheon System ASIC Design Lab.</p>	<p>VHDL ASIC NO.-115</p>																

3-State Buffer	VHDL
<p>Resolved Signal</p> <p>Data Source 2 Wire</p> <p>Resolved Signal</p> <p>3-State Buffer</p> <p>MUX</p> <p>Selected Signal Assign</p> <pre> architecture RTL1 of TRISTATE is begin TBUS<= D1 when (Y1='1') else 'Z'; TBUS<= D2 when (Y1='0' and Y2='1') else 'Z'; end RTL1; </pre>	<p>Process IF</p> <p>3-Buffer가 OFF 'Z'</p> <p>architecture RTL2 of TRISTATE is</p> <pre> begin process (Y1, D1) begin if (Y1='1') then TBUS<=D1; else TBUS<='Z'; end if; end process; process (Y1, Y2, D2) begin if (Y1='0' and Y2='1') then TBUS<=D2; else TBUS<='Z'; end if; end process; end RTL2; </pre> <p>Resolved Function</p> <p>'0' '1'</p>
<p>Univ. of Incheon System ASIC Design Lab.</p>	<p>VHDL ASIC NO.-116</p>

VHDL : ROM

ROM

 - ✍ address bus : N-bit
- ✍ data bus : M-bit



Entity Unit

```

library IEEE; use IEEE.std_logic_1164.ALL;
use IEEE.std_logic_unsigned.ALL;
entity ROM is
  generic (N: integer := 3; M: integer := 5);
  port (
    ADDR: in std_logic_vector(N-1 downto 0);
    CE_N, OE_N : in std_logic;
    DATA : out std_logic_vector(M-1 downto 0));
end ROM;
    
```

Architecture Unit

```


✍ 2
✍ ROM address Integer
architecture RTL of ROM is
  subtype WORD is
    std_logic_vector(M-1 downto 0);
  type TABLE is array(0 to 2**N-1) of WORD;
  -- type TABLE is array(0 to 2**N-1) of
  -- std_logic_vector(M-1 downto 0);
  constant ROM_DATA : TABLE :=
    TABLE( "10101", "10000", "11111", "11011",
            "10001", "01100", "00101", "10011");
begin
  process (CE_N,OE_N,ADDR) begin
    if CE_N='0' and OE_N='0' then
      DATA <=
        ROM_DATA(conv_integer(ADDR));
    else
      DATA <= (others=>'Z');
    end if;
  end process;
end RTL;
    
```



VHDL : RAM

RAM

 - ✍ address bus : 8-bit
- ✍ data bus : 8-bit



Entity Unit

```

library IEEE; use IEEE.std_logic_1164.ALL;
use IEEE.std_logic_unsigned.ALL;
entity RAM is
  port (
    ADDR: in std_logic_vector(7 downto 0);
    CE_N, RD_N, WR_N : in std_logic;
    DATA : inout
      std_logic_vector(7 downto 0));
end RAM;
    
```

Architecture Unit






```






✍ 2
✍ RAM address Integer
✍ Read Data Bus Bit
  'Z' : Resolved Signal
architecture RTL of RAM is
  subtype RAM_WORD is
    std_logic_vector(7 downto 0);
  type RAM_TABLE is array(0 to 255) of
    RAM_WORD;
  signal RAM_DATA : RAM_TABLE;
begin
  process (CE_N,RD_N,WR_N,ADDR,DATA)
    variable TMP : integer;
  begin
    DATA <= "ZZZZZZZZ";
    TMP := conv_integer(ADDR);
    if CE_N='0' and RD_N='0' then
      DATA <= RAM_DATA(TMP);
    elsif CE_N='0' and WR_N='0' then
      RAM_DATA(TMP) <= DATA;
    end if;
  end process;
end RTL;
    
```




Latch	VHDL						
<p>✂ D-Latch</p> <table border="1" style="margin-left: auto; margin-right: auto; border-collapse: collapse;"> <tr> <td style="padding: 2px;">G</td> <td style="padding: 2px;">Q(t+1)</td> </tr> <tr> <td style="padding: 2px;">0</td> <td style="padding: 2px;">Q(t)</td> </tr> <tr> <td style="padding: 2px;">1</td> <td style="padding: 2px;">D</td> </tr> </table> <div style="text-align: center; margin-top: 10px;"> </div> <p>✂ Process IF</p> <pre> architecture RTL1 of DLATCH1 is begin process (G, D) begin if G='1' then Q <= D; QBAR <= not D; end if; end process; end RTL1; </pre>	G	Q(t+1)	0	Q(t)	1	D	<p>✂ Signal Assign</p> <pre> architecture RTL2 of DLATCH1 is signal TMP : std_logic; begin TMP <= D when G='1' else TMP; Q <= TMP; QBAR <= not TMP; end RTL2; </pre> <p>✂ Latch</p> <pre> architecture RTL of EX is signal A, B, C, D, E: std_logic_vector(1 downto 0); begin process (C, D, E, EN) begin if EN='1' then A <= C; B <= D; else A <= E; end if; end process; end RTL; </pre>
G	Q(t+1)						
0	Q(t)						
1	D						
<p><small>Univ. of Incheon System ASIC Design Lab.</small></p>	<p><small>VHDL ASIC NO.-119</small></p>						

Flip-Flop	VHDL
<p>✂ Synchronous D Flip-Flop</p> <div style="text-align: center; margin-top: 10px;"> </div> <p>✂ 가 VHDL</p> <pre> A1: process (CLK) begin if (CLK='1' and CLK'event) then Q <= D; end if; end process; A2: process begin wait until CLK='1'; Q <= D; end process; </pre>	<p>✂ Asynchronous D Flip-Flop</p> <div style="text-align: center; margin-top: 10px;"> </div> <p>✂ VHDL (Synopsys Model)</p> <pre> A1: process (RESET, CLK) begin if RESET='1' then DATA <= '0'; elsif (CLK='1' and CLK'event) then DATA <= IN_DATA; end if; end process; </pre>
<p><small>Univ. of Incheon System ASIC Design Lab.</small></p>	<p><small>VHDL ASIC NO.-120</small></p>


Flip-Flop	VHDL	(1)
<p> -1</p> <pre> architecture RTL1 of EX is signal A, B: std_logic_vector(3 downto 0); begin process (CLK) begin if (CLK='1' AND CLK'EVENT) then if Q(3)/='1' then Q <= A + B; end if; end if; end process; end RTL1; </pre> <p></p>	<p> -2</p> <pre> architecture RTL2 of EX is signal A, B: std_logic_vector(3 downto 0); begin process (CLK) variable INT: std_logic_vector(3 downto 0); begin if (CLK='1' AND CLK'EVENT) then if INT(3)/='1' then INT := A + B; Q <= INT; end if; end if; end process; end RTL2; </pre> <p></p>	
		VHDL ASIC NO.-121

Flip-Flop	VHDL	(2)
<p> -3</p> <pre> architecture RTL3 of EX is begin process (RESET_N, CLK) begin if (RESET_N='0') then Q1 <= '0'; Q2 <= '0'; elsif (CLK='1' AND CLK'EVENT) then Q1 <= A and B; Q2 <= C; end if; end process; end RTL3; </pre> <p></p>	<p> -4</p> <pre> architecture RTL4 of EX is signal Q1, I2: std_logic; begin process (CLK) begin if (CLK='1' AND CLK'EVENT) then Q1 <= D; I2 <= Q1 and A; end if; end process; Q2 <= I2 and B; end RTL4; </pre> <p></p>	
		VHDL ASIC NO.-122

Variable	Signal Assignment	Flip-Flop
<ul style="list-style-type: none"> Signal Shift-Register <pre>--4 Flip-Flop library IEEE; use IEEE.std_logic_1164.all; entity SHREG4 is port (D_IN, CLK : in std_logic; D_OUT: out std_logic); end SHREG4; architecture RTL of SHREG4 is signal S0, S1, S2: std_logic; begin process (CLK) begin if (CLK='1' and CLK'event) then S0 <= D_IN; S1 <= S0; S2 <= S1; D_OUT <= S2; end if; end process; end RTL;</pre>		<ul style="list-style-type: none"> Variable Shift-Register <pre>--1 Flip-Flop process (CLK) variable S0, S1, S2: std_logic; begin if (CLK='1' and CLK'event) then S0 := D_IN; S1 := S0; S2 := S1; D_OUT <= S2; end if; end process; --4 Flip-Flop process (CLK) variable S0, S1, S2: std_logic; begin if (CLK='1' and CLK'event) then D_OUT <= S2; S2 := S1; S1 := S0; S0 := D_IN; end if; end process;</pre>


Univ. of Incheon System ASIC Design Lab.  VHDL ASIC NO.-123

Register	VHDL																														
<ul style="list-style-type: none"> Multi-Bits <ul style="list-style-type: none"> Register Shift-Register FIFO Cycle Buffer 8-Bit Register <table border="1"> <thead> <tr> <th>RESET</th> <th>LD</th> <th>ENABLE</th> <th>CLK</th> <th>REG</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>-</td> <td>-</td> <td>-</td> <td>"00000000"</td> </tr> <tr> <td>1</td> <td>1</td> <td>-</td> <td>-</td> <td>LDDATA</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> <td>-</td> <td>REG</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> <td>?(x)</td> <td>REG</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> <td>?(o)</td> <td>REGIN</td> </tr> </tbody> </table>	RESET	LD	ENABLE	CLK	REG	0	-	-	-	"00000000"	1	1	-	-	LDDATA	1	0	0	-	REG	1	0	1	?(x)	REG	1	0	1	?(o)	REGIN	<pre>library IEEE; use IEEE.std_logic_1164.ALL; entity REGISTER1 is port (RESET, LD, ENABLE, CLK : in std_logic; REGIN : in std_logic_vector(7 downto 0); REG : out std_logic_vector(7 downto 0)); end REGISTER1; architecture RTL2 of REGISTER1 is begin process (RESET, LD, CLK) begin if RESET='0' then REG <= (others =>'0'); elsif LD='1' then REG <= LDDATA; elsif ENABLE='1' then if (CLK='0' and CLK'event) then REG <= REGIN; end if; end if; end process; end RTL2;</pre>
RESET	LD	ENABLE	CLK	REG																											
0	-	-	-	"00000000"																											
1	1	-	-	LDDATA																											
1	0	0	-	REG																											
1	0	1	?(x)	REG																											
1	0	1	?(o)	REGIN																											

Univ. of Incheon System ASIC Design Lab.  VHDL ASIC NO.-124


Counter	VHDL
<p>✍ Out Mode</p> <pre> library IEEE; use IEEE.std_logic_1164.ALL; use IEEE.std_logic_unsigned.all; entity CNT8 is port (RESET,CLK: in std_logic; CNT: out std_logic_vector(2 downto 0)); end CNT8; architecture RTL1 of CNT8 is signal TMP1,TMP2: std_logic_vector(2 downto 0); begin CNT <= TMP2; TMP1 <= TMP2 + '1'; process (RESET, CLK) begin if (RESET='0') then TMP2 <= "000"; elsif (CLK='1' and CLK'event) then TMP2 <= TMP1; end if; end process; end RTL1; </pre>	<p>✍ Buffer Mode</p> <p>Signal</p> <p>✍ Buffer Mode</p> <pre> library IEEE; use IEEE.std_logic_1164.ALL; use IEEE.std_logic_unsigned.all; entity CNT8 is port (RESET,CLK: in std_logic; CNT: buffer std_logic_vector(2 downto 0)); end CNT8; architecture RTL2 of CNT8 is begin process (RESET, CLK) begin if (RESET='0') then CNT <= "000"; elsif (CLK='1' and CLK'event) then CNT <= CNT + '1'; end if; end process; end RTL2; </pre>

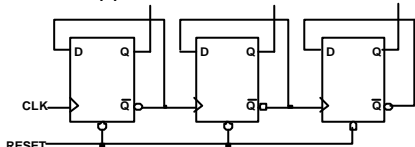


Counter	VHDL
<p>✍ 8 Ripple Counter</p>  <p>✍ Generate</p> <p>✍ D Flip-Flop</p> <pre> architecture RTL1 of DFFR is signal TMP_Q : std_logic; begin Q <= TMP_Q; QBAR <= not TMP_Q; process (RESET, CLK) begin if (RESET='0') then TMP_Q <= '0'; elsif (CLK='1' and CLK'event) then TMP_Q <= D; end if; end process; end RTL1; </pre>	<p>✍ Generate</p> <pre> architecture RTL2 of RPLCNT8 is -- Clock Wire signal CNTB: std_logic_vector(3 downto 0); -- D Flip-Flop Component component DFFR port (RESET, CLK, D : in std_logic; Q, QBAR : out std_logic); end component; -- Component Specification for U: use entity DFFR work.DFFR(RTL1); begin CNTB(0) <= CLK; GEN1: for I in 0 to 2 generate U: DFFR port map (CLK => CNTB(I), RESET => RESET, D => CNTB(I+1), Q => CNT(I), QBAR => CNTB(I+1)); end generate GEN1; end RTL2; </pre>



Finite State Machine (1)

 

 - FSM Hardware
 - Moore Type Machine
 - Mealy Type Machine



```

entity MEALYFSM is
  port (RESET, CLK, X : in std_logic;
        Z : out std_logic);
end MEALYFSM;

architecture RTL1 of MEALYFSM is
  --Symbolic State Name      Type
  type STATE is (S0, S1, S2);
  --State Signal
  signal C_STATE, N_STATE : STATE;
begin
  
```

Finite State Machine (2)

```

SYNC: process (RESET, CLK) begin
  if RESET='0' then
    C_STATE <= S0;
  elsif CLK='0' and CLK'event then
    C_STATE <= N_STATE;
  end if;
end process;

COMB : process (C_STATE, X) begin
  case C_STATE is
    when S0 =>
      Z <= '0';
      if X='0' then
        N_STATE <= S0;
      else
        N_STATE <= S1;
      end if;
    when S1 =>
      if X='0' then
        N_STATE <= S0; Z <= '0';
      else
        N_STATE <= S2; Z <= '1';
      end if;
  end case;
end process;
  
```

```

  when others =>
    if X='0' then
      N_STATE <= S0; Z <= '0';
    else
      N_STATE <= S1; Z <= '1';
    end if;
  end case;
end process;
end RTL1;
  
```

- State Code Assignment
 - Tool
 - Tool
 - Tool
 - Symbolic State Name
 - Simulation
 - Code Assign
 - Symbolic Name
 - Synthesis
 - Binary Code Assign
 - State Name
 - Binary Code Encoding

S0=(00), S1=(01), S2=(10)



Finite State Machine (3)

<p>☞ State Code가</p> <p> ☞ State Code Assignment -1</p> <pre> library IEEE; use IEEE.std_logic_1164.ALL; entity MEALYFSM is port (RESET, CLK, X : in std_logic; Z : out std_logic); end MEALYFSM; architecture RTL2 of MEALYFSM is constant S0: std_logic_vector(1 downto 0) := "00"; constant S1: std_logic_vector(1 downto 0) := "01"; constant S2: std_logic_vector(1 downto 0) := "11"; signal C_STATE, N_STATE : std_logic_vector(1 downto 0); begin -- VHDL Code end RTL2; </pre>	<p>☞ State Code Assignment -2</p> <pre> library IEEE; use IEEE.std_logic_1164.ALL; entity MEALYFSM is port (RESET, CLK, X : in std_logic; Z : out std_logic); end MEALYFSM; architecture RTL3 of MEALYFSM is --Symbolic State Name Type type STATE is (S0, S1, S2); attribute ENUM_ENCODING: string; attribute ENUM_ENCODING of STATE: type is "00 01 11"; -- State Signal signal C_STATE, N_STATE : STATE; begin -- VHDL Code end RTL3; </pre>
--	--



Chap. 4 VHDL Bench Model

Test

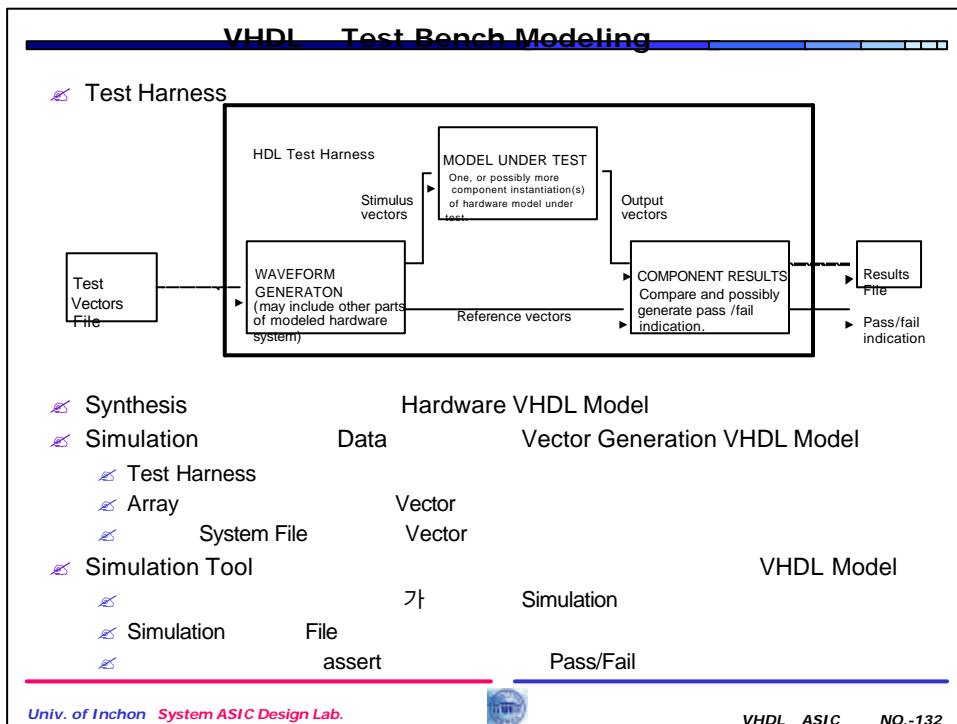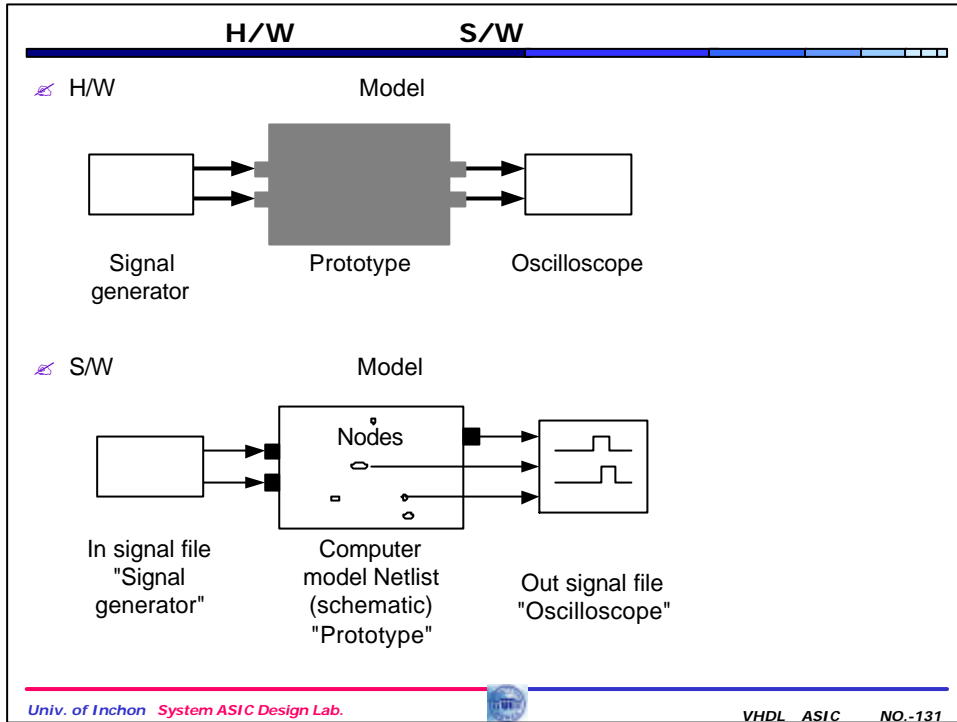


Test Vector	37 VHDL
<p>Case1 : Clock</p> <pre> signal clock, reset : std_logic := '0'; begin clock <= not clock after 20 ns; reset <= '1' after 120 ns; </pre>	
<p>case2 : Random (1)</p> <pre> x <= "00", "01" after 50 ns, "10" after 100 ns, "11" after 200 ns, "10" after 220 ns; </pre>	
<p>case3 : Random ()</p> <pre> process begin a <= '0'; b <= '1'; wait for 50 ns; a <= '1'; wait for 70 ns; b <= '0'; wait for 100 ns; a <= '0'; wait for 50 ns; end process; </pre>	
<p>Univ. of Incheon System ASIC Design Lab.</p>	<p>VHDL ASIC NO.-133</p>

Test Vector	Modeling
<pre> --9-value visibility library IEEE; use IEEE.std_logic_1164.ALL; --entity unit entity TB is port (CLOCK1 : buffer std_logic := '0'; CLOCK2, RESET1, RESET2 : out std_logic ; ENABLE : out std_logic; A_DATA, B_DATA : out std_logic_vector(7 downto 0)); end TB; --architecture unit architecture TB_A of TB is begin CLOCK1 <= not CLOCK1 after 20 ns; RESET1 <= '0', '1' after 100 ns; process begin if now = 0 ns then CLOCK2 <= '0'; wait for 250 ns; else CLOCK2 <= '1'; wait for 20 ns; CLOCK2 <= '0'; wait for 20 ns; end if; end process; </pre>	<pre> process begin A_DATA <= "00101101"; B_DATA <= "10110110"; wait for 120 ns; A_DATA <= "11011011"; wait for 30 ns; B_DATA <= "00001010"; wait for 90 ns; A_DATA <= "00011011"; wait for 150 ns; end process; process begin if now = 0 ns then RESET2 <= '0'; ENABLE <= '0'; wait for 50 ns; else RESET2 <= '1'; ENABLE <= '1'; wait for 300 ns; ENABLE <= '0' after 200 ns, '1' after 400 ns; wait for 800 ns; RESET2 <= '0', '1' after 150 ns; ENABLE <= '0' after 50 ns; wait for 200 ns; end if; end process; end TB_A; </pre>
<p>Univ. of Incheon System ASIC Design Lab.</p>	<p>VHDL ASIC NO.-134</p>

Test Vector Waveform


Test Vector Waveform

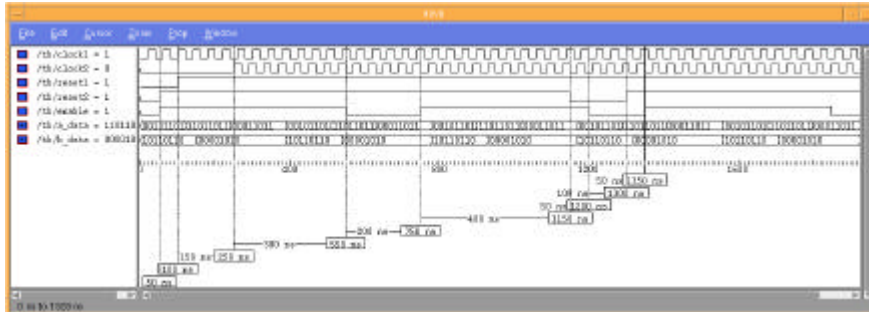

- ☞ CLOCK1, CLOCK2
- ☞ RESET1, RESET2 가
- ☞ A_DATA, B_DATA 가
- ☞ Process Data 가

-1 : Booth Multiplier

Booth Multiplier		Algorithm
A	1 0 1 1	-5
X	x 1 1 0 1	-3
Y	0 / 1 1 / 1	recorded multiplier
Add -A	0 1 0 1	
Shift	0 0 1 0 1	
Add A	+ 1 0 1 1	
	1 1 0 1 1	
Shift	1 1 1 0 1 1	
Add -A	+ 0 1 0 1	
	0 0 1 1 1 1	
Shift	0 0 0 1 1 1 1	
Shift	0 0 0 0 1 1 1 1	

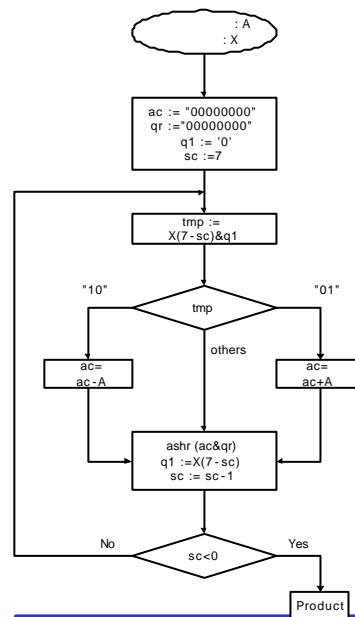

- 1 : Booth Multiplier VHDL

```

library IEEE; use IEEE.std_logic_1164.ALL;
use IEEE.numeric_std.ALL;
--
entity BOOTH is
generic (N : integer := 8);
port (RESET, CLOCK, LOAD : in std_logic;
      MULTIPLICAND, MULTIPLIER : in
        std_logic_vector(N-1 downto 0);
      PRODUCT : out
        std_logic_vector(2*N-1 downto 0));
end BOOTH;
--
architecture RTL of BOOTH is
signal Q1 : std_logic;
signal AC, BR : std_logic_vector(N-1 downto 0);
signal QR : std_logic_vector(N-1 downto 0);
signal SC : integer;
begin
process (RESET, CLOCK)
variable TMP_AC : std_logic_vector(N-1 downto 0);
begin
if RESET='0' then
BR <= (OTHERS => '0');
QR <= (OTHERS => '0');
AC <= (OTHERS => '0');
Q1 <= '0';
SC <= N;
PRODUCT <= (OTHERS => '0');
elsif (CLOCK='1' AND CLOCK'event) then
if LOAD='1' then
BR <= MULTIPLICAND;
QR <= MULTIPLIER;
AC <= (OTHERS => '0');
Q1 <= '0';
SC <= N;
PRODUCT <= (OTHERS => '0');
else
if (SC=0) then
PRODUCT <= AC & QR;
else
if QR(0)='0' and Q1='1' then
TMP_AC := AC + BR;
elsif QR(0)='1' and Q1='0' then
TMP_AC := AC + not BR + '1';
else
TMP_AC := AC;
end if;
end if;
Q1 <= QR(0);
QR <= TMP_AC(0) & QR(N-1 downto 1);
AC <= TMP_AC(N-1) & TMP_AC(N-1 downto 1);
SC <= SC - 1;
end if;
end if;
end process;
end RTL;
--

```



- 1 : Test Bench

```

Vector
library IEEE; use IEEE.std_logic_1164.ALL;
library IEEE.numeric_std.ALL;
entity VEC_GEN is
port (CLOCK, RESET, LOAD : out std_logic;
      A_PORT, B_PORT : out std_logic_vector(7 downto 0));
end VEC_GEN;
architecture VEC_GEN_A of VEC_GEN is
signal CLOCK_S : std_logic := '0';
begin
RESET <= '1' after 50 ns;
CLOCK_S <= not CLOCK_S after 2 ns;
CLOCK <= CLOCK_S;
LOAD <= '0', '1' after 20 ns, '0' after 70 ns,
      '1' after 210 ns, '0' after 250 ns,
      '1' after 390 ns, '0' after 430 ns,
      '1' after 570 ns, '0' after 610 ns;
A_PORT_DRV : process begin
A_PORT <= "00000101"; wait for 200 NS;
A_PORT <= "11111011"; wait for 400 NS;
end process;
B_PORT_DRV : process begin
B_PORT <= "00000011"; wait for 400 NS;
B_PORT <= "11111101"; wait for 400 NS;
end process;
end VEC_GEN_A;

Test Bench
library IEEE; use IEEE.std_logic_1164.ALL;
use IEEE.numeric_std.ALL;
entity TB_BOOTH1 is end TB_BOOTH1;
architecture TB_BOOTH1_A of TB_BOOTH1 is
component BOOTH
generic (n : integer := 8);
port (RESET, CLOCK, LOAD : in std_logic;
      MULTIPLICAND, MULTIPLIER : in
        std_logic_vector(n-1 downto 0);
      PRODUCT : out
        std_logic_vector(2*n-1 downto 0));
end component;
-- Vector Generation Block
signal A_PORT, B_PORT : std_logic_vector(7 downto 0);
signal MUL_OUT : std_logic_vector(15 downto 0);
signal RESET, CLOCK, LOAD : std_logic;
for u0 : BOOTH use entity work.BOOTH(RTL);
for u1 : VEC_GEN use entity
work.VEC_GEN(VEC_GEN_A);
begin
u0 : BOOTH port map(RESET, CLOCK, LOAD,
A_PORT, B_PORT, MUL_OUT);
u1 : VEC_GEN port map (CLOCK, RESET, LOAD,
A_PORT, B_PORT );
end TB_BOOTH1_A;

```



- 1 : File

Test Bench

Test Bench

```
library IEEE; use IEEE.std_logic_1164.ALL;
use IEEE.std_logic_signed.ALL;
use IEEE.std_logic_textio.ALL; use std.textio.ALL;
entity TB_BOOTH3 is end TB_BOOTH3;
architecture TB_BOOTH3_A of TB_BOOTH3 is
  component BOOTH
    generic (n : integer := 8);
    port ( RESET, CLOCK, LOAD : in std_logic;
          MULTIPLICAND, MULTIPLIER : in
            std_logic_vector(n-1 downto 0);
          PRODUCT: out std_logic_vector(2*n-1 downto
            0));
  end component;
  signal A_PORT, B_PORT: std_logic_vector(7 downto
    0);
  signal MUL_OUT: std_logic_vector(15 downto 0);
  signal RESET, CLOCK, LOAD: std_logic := '0';
  for u0 : BOOTH use entity work.BOOTH(RTL);
begin
  RESET <= '1' after 50 ns;
  CLOCK <= not CLOCK after 2 ns;
  u0 : BOOTH port map(RESET, CLOCK, LOAD,
    A_PORT, B_PORT, MUL_OUT);
```

```
process
  file VECTOR_FILE : text is in "vectors";
  variable LOAD_V : std_logic;
  variable A_PORT_V, B_PORT_V :
    std_logic_vector(7 downto 0);
  variable DELAY : time;
  variable L : line;
  variable GOOD_NUMBER : boolean;
begin
  while not endfile(VECTOR_FILE) loop
    readline ( VECTOR_FILE, L );
    read (L, DELAY, GOOD => GOOD_NUMBER);
    next when not GOOD_NUMBER;
    READ(L, LOAD_V);
    READ(L, A_PORT_V);
    READ(L, B_PORT_V);
    WAIT FOR delay - now;
    LOAD <= LOAD_V;
    A_PORT <= A_PORT_V;
    B_PORT <= B_PORT_V;
  end loop;
  wait;
end process;
```



- 1 : File

Test Bench

```
process
  file TABLE_FILE : text is out "results";
  variable TABLE_LINE : line;
begin
  wait on MUL_OUT;
  write ( TABLE_LINE, now, RIGHT, 10, ns );
  write ( TABLE_LINE, '' );
  write ( TABLE_LINE, MUL_OUT(15) );
  write ( TABLE_LINE, MUL_OUT(14) );
  write ( TABLE_LINE, MUL_OUT(13) );
  write ( TABLE_LINE, MUL_OUT(12) );
  write ( TABLE_LINE, MUL_OUT(11) );
  write ( TABLE_LINE, MUL_OUT(10) );
  write ( TABLE_LINE, MUL_OUT(9) );
  write ( TABLE_LINE, MUL_OUT(8) );
  write ( TABLE_LINE, MUL_OUT(7) );
  write ( TABLE_LINE, MUL_OUT(6) );
  write ( TABLE_LINE, MUL_OUT(5) );
  write ( TABLE_LINE, MUL_OUT(4) );
  write ( TABLE_LINE, MUL_OUT(3) );
  write ( TABLE_LINE, MUL_OUT(2) );
  write ( TABLE_LINE, MUL_OUT(1) );
  write ( TABLE_LINE, MUL_OUT(0) );
  writeln ( TABLE_FILE, TABLE_LINE );
end process;
end TB_BOOTH3_A;
```

Stimulus Vector File : "vectors"

0 NS	0 00000101 00000011
20 NS	1 00000101 00000011
70 NS	0 00000101 00000011
200 NS	0 11111011 00000011
210 NS	1 11111011 00000011
250 NS	0 11111011 00000011
390 NS	1 11111011 00000011
400 NS	1 11111011 11111101
430 NS	0 11111011 11111101
570 NS	1 11111011 11111101
600 NS	1 00000101 11111101
610 NS	0 00000101 11111101
800 NS	0 11111011 00000011

File : "results"

0 NS	0000000000000000
106 NS	0000000000001111
214 NS	0000000000000000
286 NS	1111111111110001
394 NS	0000000000000000
466 NS	0000000000001111
574 NS	0000000000000000
646 NS	1111111111110001



- 1 : FPGA Prototyping

Booth Multiplier

FPGA

Board

